

Synchronous, Phase Modulated, Full Bridge Converter Targets Isolated High Power Applications

by Kurk Mathews

Introduction

In networking and telecom equipment, power supplies provide isolated low voltage outputs from the 48V input supply rail, with the added requirements of high efficiency (to reduce heat dissipation) and low component height. These requirements become even more difficult to meet with increased power levels, because of the corresponding component power dissipation and increased transformer size. Simple power supply topologies give way to more complex single and two-stage approaches that focus on transformer and semiconductor utilization.

One such approach, the phase modulated full bridge converter, is a popular choice for high power supplies. Unfortunately, until now, there has not been a controller that offers both the flexibility in timing control and features (such as synchronous rectifier outputs) to manage a variety of high power applications. The new LTC3722-1 current-mode controller

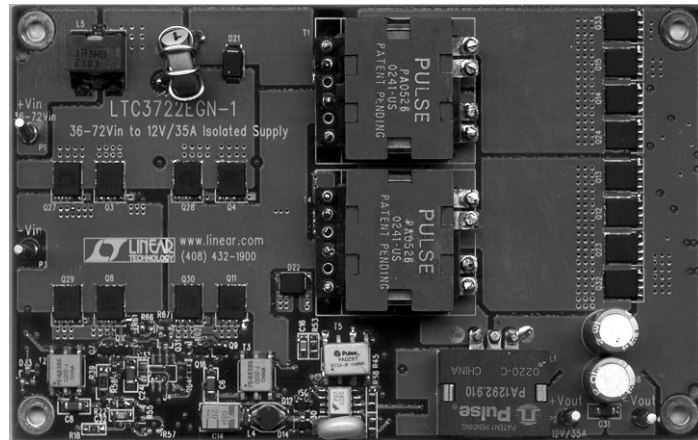


Figure 1. LTC3722-1 36-72V input to 12V/35A isolated power supply

is designed specifically with these issues in mind, providing a full-featured controller for high power, phase modulated, full bridge converters.

12V Isolated Converter

Figures 1 and 2 show a 36V-72V input to isolated 12V at 35A supply using the LTC3722EGN-1 (24-lead SSOP) and LTC4440 high side drivers. The low profile design features surface mount power MOSFETs and planar transformers (less than 0.4" high) configured in a parallel/series configuration. With a 48V input, this circuit has a typical full load (35A) efficiency of 93%. The PCB board shown in Figure 1 is 3"x 5", and with 200 linear feet per minute of airflow provides full load operation from 48V input to 50°C ambient without the use of a heat sink. The actual PCB area can be reduced further (depending on airflow and ambient temperature) when used as part of a large system board.

Even with 12V output, the synchronous rectifiers reduce the power dissipation in the secondary rectifiers. The output of 12V is chosen here because it is a good intermediate bus voltage, but the circuit is easily modi-

fied to meet other input or output voltages. For example, applications not requiring the full input voltage range or tight regulation could further optimize transformer and semiconductor utilization resulting in increased efficiency.

Operation

The start-up of the circuit in Figure 2 begins with C14 trickle charging via R29 and Q41's base-collector junction until U2's V_{IN} pin reaches 10.2V (the internal shunt regulator voltage). Assuming the undervoltage lockout pin (UVLO) is above a 5V threshold, switching begins. C14 keeps the U2's V_{IN} pin above its 6.0V shutdown threshold until a bias winding on T4 (along with D12, D14 and L4) takes over. U4 and U5 provide the level translation for the two high side switches. U2's OUTE and OUTF pins provide synchronous timing signals to the output rectifiers gate drive transformer T5 and the LTC1693 gate driver. The loop is closed by U3, the LT1431 programmable reference, and optocoupler ISO1.

Operation of the phase modulated full bridge converter is similar to a conventional full bridge converter in

continued on page 35

DESIGN IDEAS

Synchronous, Phase Modulated, Full Bridge Converter Targets Isolated High Power Applications

Kurk Mathews

Monolithic Buck-Boost Converter Provides 1A at 3.3V without Schottky Diodes

Mark Jordan

Inductorless, Efficient Step-Down DC/DC Converter Provides Dual Low Noise Outputs in Space-Constrained Designs.....

Bill Walter

Using Current Sensing Resistors with Hot Swap Controllers and Current Mode Voltage Regulators..

Eric Trelewicz

Complete USB Solution Provides PowerPath Control and Input Current Limiting while Charging a Li-Ion Battery

Trevor Barcelo

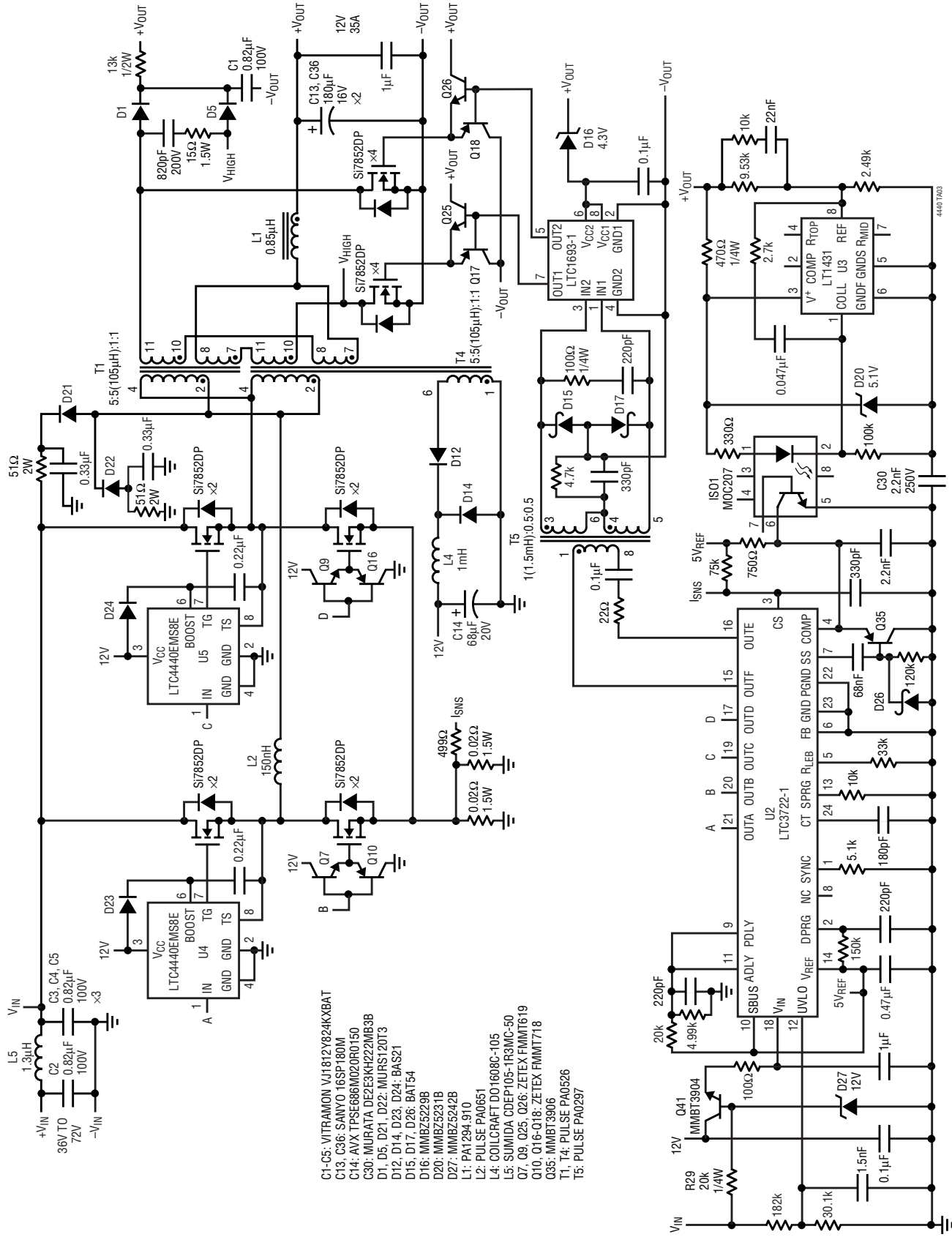


Figure 2. LTC3722-1 36-72V input to 12V/35A isolated synchronous full bridge power supply

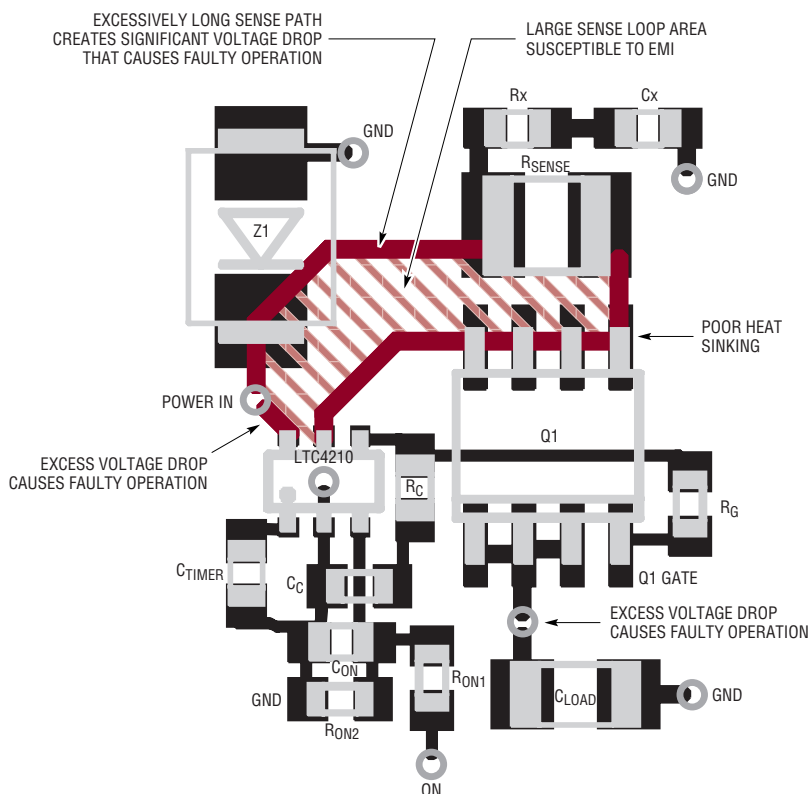



Figure 3. Example of layout that can reduce the accuracy of Kelvin sensing. The problems shown here include: excess length of thin high resistance track in series with sense resistor, inadequate heat sinking on Q1, and an insufficient number of vias for input power and output load connections.

resistors. The use of a 4-terminal resistor forces the auto router to make a correct Kelvin connection to the cur-

rent sense resistor. But this alone is not enough. High speed switch mode power supplies have a high dI/dt path

that can inductively couple with the sense loop and also cause malfunction. To minimize inductive coupling, the Kelvin sense circuit must exhibit minimal loop area.

Setting the Proper Constraints in an Auto-Router

Set the auto-router constraints to route the Kelvin sense connections as a differential pair to keep the connections side by side and close together. Use maximum length constraints to prevent the connections from wandering too far from the direct path. Constrain the connection to the component layer on a multi-layer PCB board to prevent unwanted vias in this critical connection path. Although the proper choice of sense resistor and layout constraints can mitigate many of the PCB layout pitfalls, in the end it's up to the designer to carefully check the layout. 

Notes


- ¹ Some sources of 4-terminal Kelvin sensed resistors include:
- www.Caddock.com
 - www.IMS-Resistors.com
 - www.IRCtt.com
 - www.Vishay.com

LTC3722, continued from page 30

that power is delivered when diagonal switches are on. It differs in that during the free-wheeling portion of the switching cycle, either the top or bottom switches of the bridge remain on. This provides for recovery of parasitic energy and zero-voltage turn-on transitions for the primary switches. The LTC3722-1 can be configured to provide adaptive (with programmable time-out) or fixed delay control for zero voltage switching operation. In adaptive DirectSense™ mode, the

turn-on timing adjusts automatically by sensing the transition voltages on the bridge legs, eliminating external trims. This provides accurate zero voltage transition timing with changes in input voltage, output load and circuit parasitics. Fixed (or manual) delay control is also available, which allows for fixed transition delays or even custom dynamic timing schemes. The LTC3722-1 also features adjustable synchronous rectifier timing.

Conclusion

The new LTC3722-1 current-mode controller provides a wealth of features targeted at high power isolated full bridge applications, including flexible timing control, synchronous rectifier outputs, under-voltage lockout, programmable slope compensation and current mode leading edge blanking. 

LTC4302, continued from page 16

Summary

The LTC4302-1/LTC4302-2 addressable 2-wire bus buffers ease the practical issues associated with complex 2-wire bus systems. They allow I/O cards to be hot-plugged

into live systems and break one large capacitive bus into several smaller ones, while still passing the SDA and SCL signals to every device in the system. They can also connect and disconnect different bus segments

at different times, providing nested addressing capability and easing the debugging process during stuck low situations. 