

Figure 4a. This circuit resets the circuit breaker after a current fault.

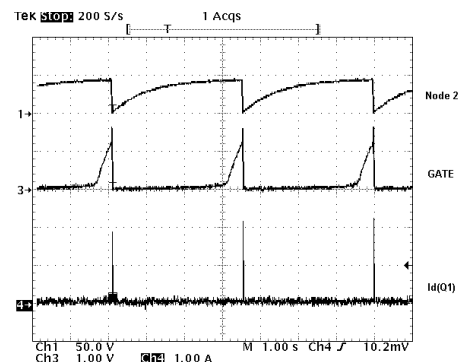


Figure 4b. Waveforms of Figure 4a's circuit

resistor between the V_{EE} and SENSE pins, the circuit breaker will be tripped whenever the voltage across the sense resistor is greater than 50mV for more than 3 μ s, as shown in Figure 3.

When the circuit breaker trips, the GATE pin is immediately pulled to V_{EE} and the external N-channel MOSFET is turned off. The GATE pin will remain low until the circuit breaker is reset by pulling UV low then high or cycling power to the part. A circuit that automatically resets the circuit breaker after a current fault is shown in figure 4.

Transistors Q2 and Q3, along with R7, R8, C4 and D1, form a programmable one-shot circuit. Before a short occurs, the GATE pin is pulled high and Q3 is turned on, pulling node 2 to V_{EE} . Resistor R8 turns off Q2. When a short occurs, the GATE pin is pulled low and Q3 turns off. Node 2 starts to charge C4, and Q2 turns on, pulling the UV pin low and resetting the circuit breaker. As soon as C4 is fully

charged, R8 turns off Q2, UV goes high and the voltage on the GATE starts to increase. Q3 turns back on and quickly pulls node 2 back to V_{EE} . Diode D1 clamps node 3 one diode drop below V_{EE} . The duty cycle is set to 10% to prevent Q1 from overheating.

Undervoltage and Overvoltage Detection

The UV (3) and OV (2) pins can be used to detect undervoltage and overvoltage conditions at the power supply input. The UV and OV pins are internally connected to analog comparators with 20mV of hysteresis. When the UV pin falls below its threshold or the OV pin rises above its threshold, the GATE pin is immediately pulled low. The GATE pin will be held low until UV is high and OV is low.

The undervoltage and overvoltage trip voltages can be programmed using a 3-resistor-divider, as shown in Figure 5.

With $R4 = 562k$, $R5 = 9.09k$ and $R6 = 10k$, the undervoltage threshold is set to 37V and the overvoltage threshold is set to 71V.

PWRGD/ \overline{PWRGD} Output

The PWRGD/ \overline{PWRGD} output can be used to directly enable a power module when the input voltage to the module is within tolerance. The LT1640H has a PWRGD output for modules with an active-high enable input, and the LT1640L has a PWRGD output for modules with an active-low enable input.

When the DRAIN pin of the LT1640H is more than V_{PG} (1.4V) above V_{EE} (see Figure 6), internal transistor Q3 is turned off and R7 and Q2 clamp the PWRGD pin one diode drop ($\sim 0.7V$) above the DRAIN pin. Transistor Q2 sinks the module's pull-up current and the module turns off.

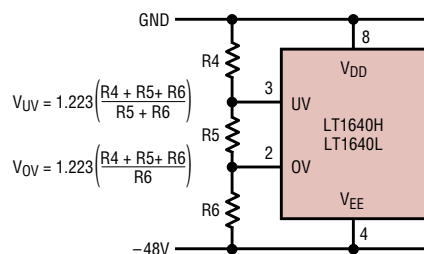


Figure 5. Undervoltage and overvoltage sensing

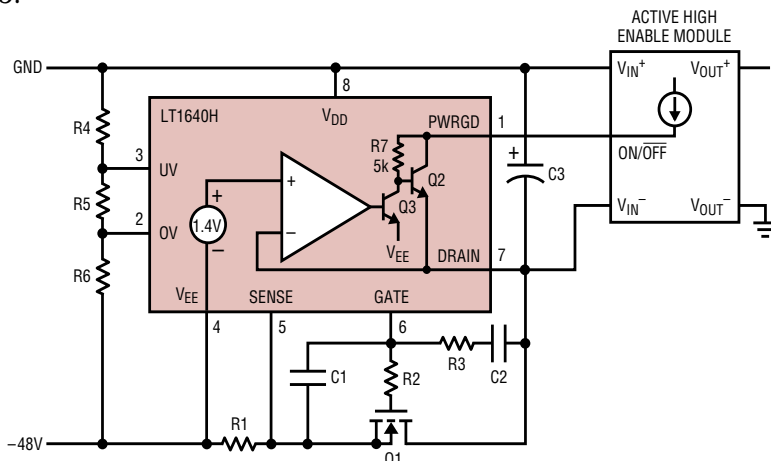


Figure 6. Active-high enable module

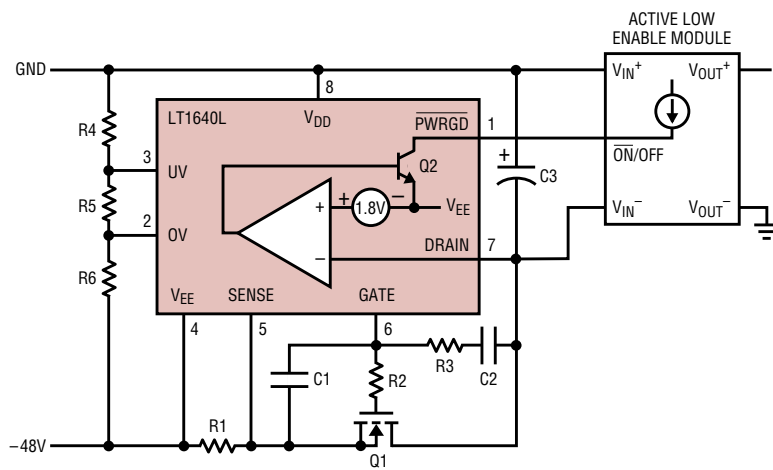


Figure 7. Active-low enable module

When the DRAIN pin drops below V_{PG} , Q3 will turn on, shorting the bottom of R7 to V_{EE} and turning Q2 off. The pull-up current in the module then flows through the R7, pulling the PWRGD pin high and enabling the module.

When the DRAIN pin of the LT1640L is more than V_{PG} (1.4V) above V_{EE} , the internal pull-down transistor, Q2, is off and the PWRGD pin is in high impedance state (see Figure 7). The PWRGD pin will be pulled high by the module's internal pull-up current source, turning the module off. When the DRAIN pin drops below V_{PG} , Q2 will turn on, and the PWRGD pin will be pulled low, enabling the module.


The PWRGD signal can also be used to turn on an LED or optoisolator to indicate that the power is good, as shown in Figure 8.

Gate Pin Voltage Regulation

When the supply voltage to the chip is more than 15.5V, the GATE pin voltage is regulated at 13.5V above V_{EE} . If the supply voltage is less than 15.5V,

the GATE voltage will be about 2V below the supply voltage. At the minimum 10V supply voltage, the gate voltage is guaranteed to be greater than 6V and no greater than 18V for supply voltages up to 80V.

Conclusion

LT1640 provides a simple and flexible solution for hot swap applications. It is the first part that allows system designers to connect an 80V supply directly to the chip without any voltage step-down circuitry. It can be programmed to control the output voltage slew up rate and the inrush current. It has programmable under-voltage and overvoltage protection, and the PWRGD/PWRGD output can be tied directly to a power-module enable pin. The LT1640 simplifies the design of high voltage hot-swap control systems and combines all of these features in an 8-pin SO/PDIP package. 

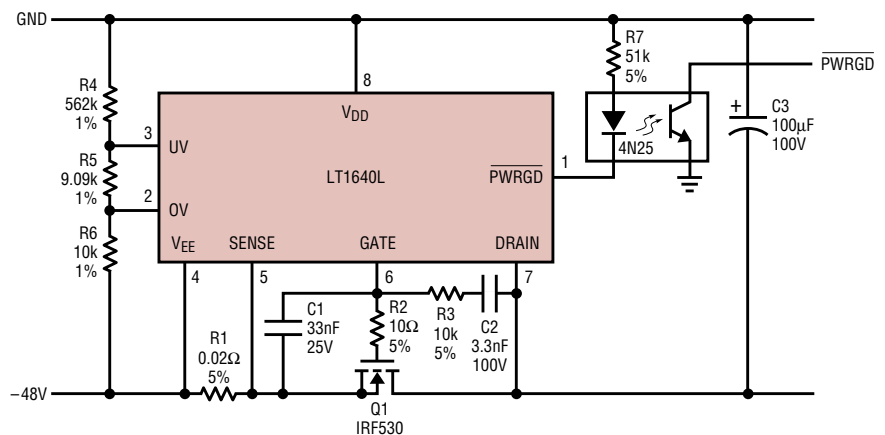


Figure 8. Using PWRGD to drive an optoisolator

Authors can be contacted
at (408) 432-1900

for
the latest information
on LTC products,
visit
www.linear-tech.com