

IN THIS ISSUE...

COVER ARTICLE

Photoflash Capacitor Chargers Fit into Tight Spots 1
Albert Wu

Issue Highlights 2

LTC® in the News 2

DESIGN FEATURES

Digital Programmable Oscillator Is Smaller, Sturdier and More Versatile than Crystal Oscillators 7
Albert Huntington

Hot Swap™ Controller with Power-Up Timeout Function Simplifies Hot Swapping Boards with Multiple Power Supplies 10
Anthony Ng and YK Sim

Low Voltage Wizardry Provides the Ultimate Power-On Reset Circuit ... 14
Bob Jurgilewicz

New Power for Ethernet—Disconnect and Clean Up (Epilogue to a 3-part series) 17
Jacob Herbold

Save Board Space with a High Efficiency Dual Synchronous, 600mA, 1.5MHz Step-Down DC/DC Regulator 19
Damon Lee

White LED Driver Minimizes Space, Maximizes Efficiency and Flexibility 22
Steven Martin

High Input Voltage Monolithic Switcher Steps Up and Down Using Single Inductor 24
Jay Celani

Hot Swap Controller Enforces Tracking in Split Supply Systems 28
Ted Henderson

Voltage Margining Made Easy 31
Jeff Heath

DESIGN IDEAS

..... 33-37
(complete list on page 33)

New Device Cameos 38

Design Tools 39

Sales Offices 40

Photoflash Capacitor Chargers Fit into Tight Spots

by Albert Wu

Introduction

Take a walk through any electronics retailer and you will notice an obvious trend: Cameras are being added to PDAs, cell phones and other portable devices. This is due, of course, to shrinking electronics required for digital imaging. Even as imaging electronics shrink, the imaging pixel count grows. The corresponding increase in image quality demands a corresponding improvement in photoflash technology. LED-based photoflash units are certainly compact enough to fit in the smallest devices, but LED units cannot meet the light output and spectral quality required of one megapixel or higher sensors. A xenon-bulb based flash unit offers better performance, but traditionally takes more space. Now there is a way to fit a xenon-bulb photoflash unit into the

tightest spaces. The solution is to use one of Linear Technology's LT®3468 photoflash capacitor chargers.

The LT3468 series is available in a 5-Lead ThinSOT™ package. All output voltage detection is implemented inside the part, substantially reducing external parts count to a mere four components. A new patented control technique allows the use of ultra-small transformers while maintaining high efficiency. Imaging devices using these parts can save significant space while still achieving well controlled battery current, fast charge times and high efficiency.

Overview

A typical application for the LT3468 is shown in Figure 1a. The high level of

continued on page 3

DANGER HIGH VOLTAGE—OPERATION BY HIGH VOLTAGE TRAINED PERSONNEL ONLY

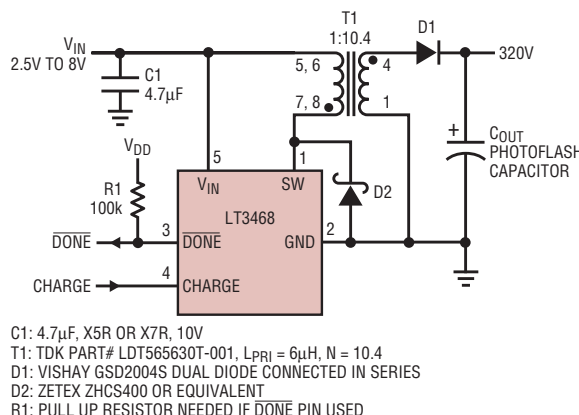


Figure 1a. Compact, 320V photoflash capacitor charging circuit needs no zener

LT3468, continued from page 1

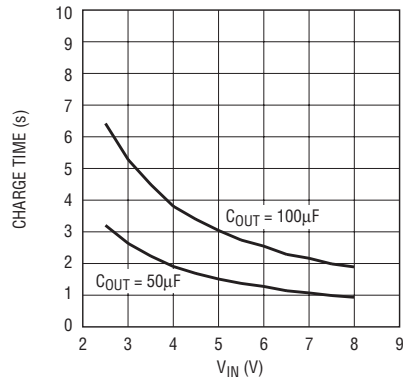


Figure 1b. Charge times

integration inside the part results in a very simple circuit that takes little valuable board space. Figure 1c shows an entire charging circuit fitting into 80mm². The tallest component on

the board is the transformer, which is only 3mm in height. Despite the tiny components, charge time is excellent due to the high power, integrated low resistance NPN power switch.

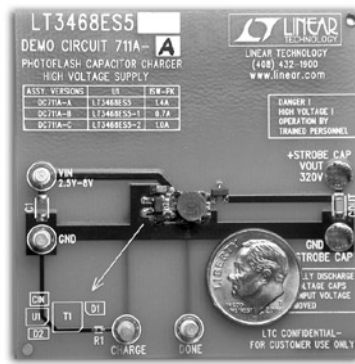


Figure 1c. The LT3468 makes it possible to fit an entire photoflash charging circuit into 80mm²

The LT3468-1 is a lower current version of the LT3468. Figure 2a shows a typical application circuit while Figure 2b shows the charge time. The input current for the LT3468-1 is typically 250mA, while that of the LT3468 is about 550mA.

Operation

To better understand the operation of the part, refer to Figure 3 for the following overview. Note that the only difference between the LT3468 and the LT3468-1 is the switch current limit (1.4A for the LT3468, 0.7A for the LT3468-1). A low-to-high transition on the CHARGE pin initiates the part. An edge triggered one-shot triggered by the CHARGE pin puts the various latches inside the part into the proper state.

DANGER HIGH VOLTAGE—OPERATION BY HIGH VOLTAGE TRAINED PERSONNEL ONLY

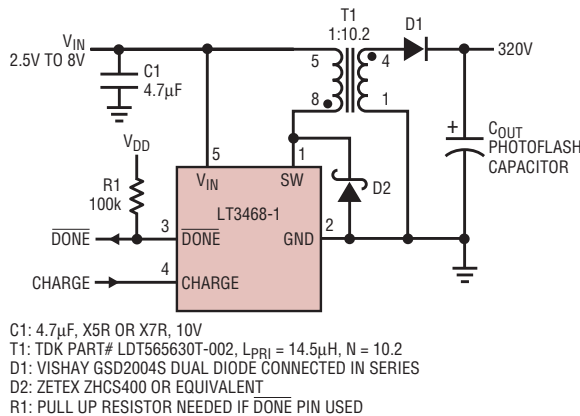


Figure 2a. LT3468-1 photoflash circuit uses tiny 3mm tall transformer

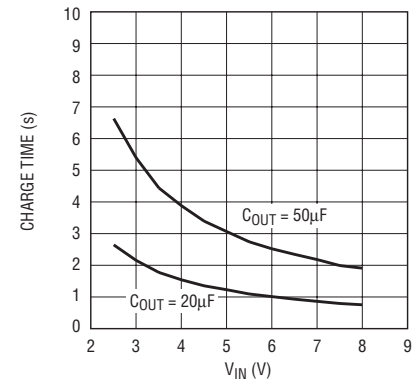


Figure 2b. Charge time

Table 1. Comparison chart for Linear Technology's photoflash charger parts

	LT3468	LT3468-1	LT3420	LT3420-1
Peak SW Current (A)	1.4	0.7	1.4	1.0
Secondary Current at SW Turn On (mA)	0		40	20
Average Input Current (mA) (V _{IN} = 3.3V, V _{OUT} = 300V)	550	250	840	500
Minimum Battery Voltage (V)	2.5		1.8	
Integrated Output Detection?	Yes		No	
Automatic Refresh?	No		Yes	
Common Battery Combinations	1–2 Li-ion cell 4 AA cells 4 NIMH cells		1–2 Li-ion cell 2–4 AA cells 2–4 NIMH cells	
Package	TSOT-5L		MSOP-10L	

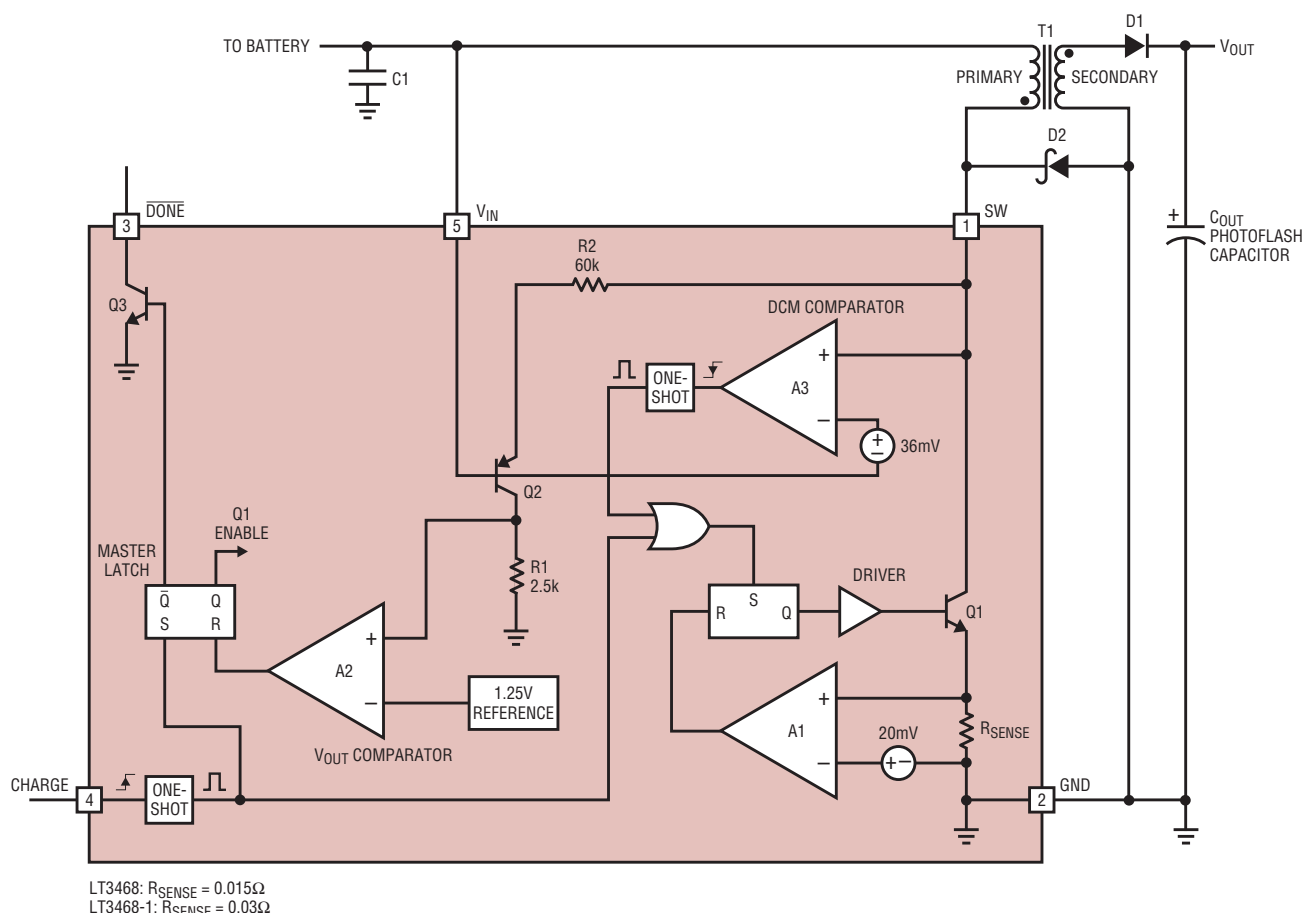


Figure 3. Block diagram of the LT3468

The part begins charging by turning on the power NPN transistor $Q1$. With $Q1$ on, the current in the primary of the flyback transformer increases. When it reaches the current limit, $Q1$ is turned off and the secondary of the transformer delivers current to the photoflash capacitor via diode $D1$. During this time, the voltage on the SW pin is proportional to the output voltage. Since the SW pin is higher than V_{IN} by an amount roughly equal to $(V_{OUT} + 2 \cdot V_D)/N$, the output of the DCM Comparator is high. In this equation, V_{OUT} is the photoflash capacitor voltage, V_D is the rectifying diode forward drop, and N is the turns ratio of the transformer.

Once the current in the secondary of the transformer decays to zero, the voltage on the SW pin collapses to V_{IN} , or lower. As a result, the output of the DCM comparator goes low, which triggers the one-shot. This leads to $Q1$ turning on again and the cycle repeats.

Output voltage detection is accom-

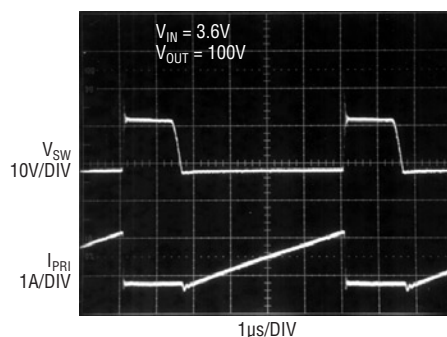


Figure 4a. LT3468 switching waveform at 100V output

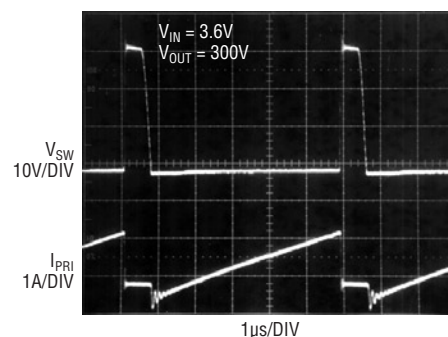


Figure 4b. LT3468 switching waveform at 300V output

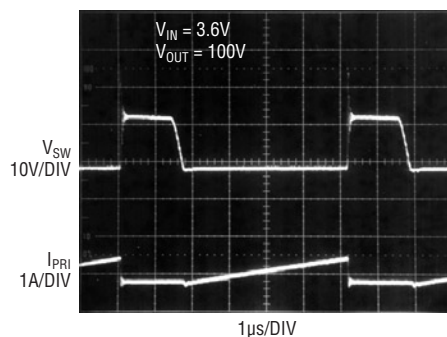


Figure 4c. LT3468-1 switching waveform at 100V output

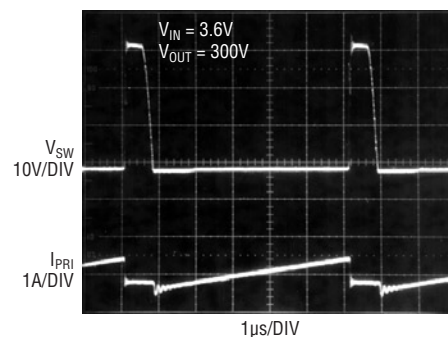


Figure 4d. LT3468-1 switching waveform at 300V output

plished via comparator A2. When the SW pin is 31.5V higher than V_{IN} on any cycle, the output of A2 goes high. This resets the master latch and the part stops delivering power to the photoflash capacitor. Power delivery can only restart by taking the CHARGE pin low and then high.

Note that the flux in the flyback transformer is brought to zero on each switching cycle. This is generally referred to as boundary mode since the transformer is operated in between continuous conduction mode and discontinuous conduction mode (CCM and DCM respectively). When the CHARGE pin is forced low at anytime, the LT3468 ceases power delivery and goes into shutdown mode, thus reducing quiescent current to less than 1 μ A. Figure 4 shows some typical switching waveforms for the LT3468 and LT3468-1.

Which Part to Use?

The LT3468 and LT3468-1 round out LinearTechnology's photoflash capacitor charger line to four chargers that can suit just about any photoflash need: the LT3468, LT3468-1, LT3420, and the LT3420-1. Table 1 shows the major functional differences between these four parts.

Choosing a device is a matter of balancing the inherent trade-off between average input current and charge time.

For a given photoflash capacitor size, the device which results in the highest average input current offers the fastest charge time. The limit on how much current the photoflash charger can draw is usually set by the batteries, and how much load they can handle. The LT3420 offers the fastest charge times of the chargers discussed here.

The following equations predict the charge times (T) in seconds for the four parts:

LT3468:

$$T = \frac{C_{OUT} \cdot (V_{OUT(FINAL)}^2 - V_{OUT(INIT)}^2)}{0.65 \cdot V_{IN}}$$

LT3468-1:

$$T = \frac{C_{OUT} \cdot (V_{OUT(FINAL)}^2 - V_{OUT(INIT)}^2)}{0.32 \cdot V_{IN}}$$

LT3420:

$$T = \frac{C_{OUT} \cdot (V_{OUT(FINAL)}^2 - V_{OUT(INIT)}^2)}{1.2 \cdot V_{IN}}$$

LT3420-1:

$$T = \frac{C_{OUT} \cdot (V_{OUT(FINAL)}^2 - V_{OUT(INIT)}^2)}{0.55 \cdot V_{IN}}$$

where C_{OUT} is the value of the photoflash capacitor in Farads, $V_{OUT-FINAL}$ is the target output voltage, $V_{OUT-INIT}$ is

the initial output voltage, and V_{IN} is the battery or input voltage to which the flyback transformer is connected.

These equations are developed for specific transformers, namely the TDK LDT565630T-001 for the LT3468, the TDK LDT565630T-002 for the LT3468-1, the TDK SRW10EPC-U01H003 for the LT3420 and the Kijima Musen SBL-5.6S-2 for the LT3420-1. If other transformers are used, the constant in the denominator of each the above equations changes slightly because of differing transformer efficiencies.

Generally speaking, the LT3468 is used for photoflash capacitors in the 80 μ F to 160 μ F range commonly found in mid- to high-end digital cameras. The LT3468-1 is used for photoflash capacitors in the 10 μ F-80 μ F range, which are likely to be required in ultra small digital cameras and cell phone-based cameras. For designs required to operate from 2AA cells, the LT3420 and LT3420-1 are the right choice, as they are designed to operate on a battery voltage down to 1.8V.

Output Voltage Detection

A major benefit of the LT3468 and LT3468-1 is the complete integration of output voltage detection inside the part. The output voltage is sensed via the flyback transformer as described in the operation section above. The

Table 2. Pre-designed transformers and typical specifications (unless otherwise noted)

For Use With	Transformer Name	Size (mm) (W × L × H)	L _{PRI} (μ H)	L _{PRI} - Leakage (nH)	N	R _{PRI} (m Ω)	R _{SEC} (Ω)	Vendor
LT3468 LT3468-1	SBL-5.6-1 SBL-5.6S-1	5.6 × 8.5 × 4.0 5.6 × 8.5 × 3.0	10 24	200 Max 400 Max	10.2 10.2	103 305	26 55	Kijima Musen Hong Kong Office 852-2489-8266 (ph) kijimahk@netvigatator.com (email)
LT3468 LT3468-1	LDT565630T-001 LDT565630T-002	5.8 × 5.8 × 3.0 5.8 × 5.8 × 3.0	6 14.5	200 Max 500 Max	10.4 10.2	100 Max 240 Max	10 Max 16.5 Max	TDK Chicago Sales Office (847) 803-6100 (ph) www.components.tdk.com
LT3468/LT3468-1 LT3468-1	T-15-089 T-15-083	6.4 × 7.7 × 4.0 8.0 × 8.9 × 2.0	12 20	400 Max 500 Max	10.2 10.26	211 Max 75 Max	27 Max 35 Max	Tokyo Coil Engineering Japan Office 0426-56-6336(ph) www.tokyo-coil.co.jp

Table 3a. Performance comparison of LT3468 and two microprocessor-controlled photoflash charging units from actual digital cameras

	LT3468	μ P-Controlled Flyback #1	μ P-Controlled Flyback #2
Charge Time (seconds) ($V_{IN} = 3V$, V_{OUT} charged from 50V to 320V, 120 μ F photoflash capacitor)	6.3	13.6	7.5
Average Input Current (mA)	500	430	750

Table 3b. Normalized performance comparison of LT3468 and two microprocessor-controlled photoflash charging units from actual digital cameras

	LT3468	μ P-Controlled Flyback #1	μ P-Controlled Flyback #2
Normalized Charge Time (seconds) ($V_{IN} = 3V$, V_{OUT} charged from 50V to 320V, 120 μ F photoflash capacitor)	6.3	11.7	11.2
Average Input Current (mA) Normalized to 500mA	500		

output voltage is thus set by the turns ratio, N , of the transformer. Choose N with the following equation:

$N = (V_{OUT} + 2)/31.5$, where V_{OUT} is the desired output voltage.

Because most of the output detection circuitry, other than the transformer, is integrated inside the IC, the accuracy of the output detection can be very good. The 31.5V comparator voltage is precision trimmed and is specified at $\pm 1.6\%$ over the full operating temperature range. To find the worst case deviation on the output voltage, simply add this deviation to the worst case deviation in the turns

ratio N of the transformer. Typical guaranteed deviations of N are in the 2%–3% range, although there is likely much room for improvement here. Consult your transformer vendor for more information. Figure 5 shows a histogram of the V_{OUT} distribution for a sample (~100 units) of LT3468 prototype boards. As you can see, the distribution is tight in a range of $\pm 5V$, which is equivalent to a tolerance under $\pm 1.5\%$

Pre-Designed Transformers

Linear Technology Corporation has worked with several transformer

manufacturers to produce transformer designs that are optimized for the LT3468 and LT3468-1. In most applications, these transformers, shown in Table 2, will suffice. Of particular interest are the ultra small transformers now available—as small as 5.8mm \times 5.8mm \times 3.0mm—which still achieve excellent efficiency and charge time.

Comparison of the LT3468 and LT3468-1 to Discrete Photoflash Chargers

There are numerous benefits to using the LT3468 series of parts—best seen when the LT3468 series is compared to the current method used by many digital camera manufacturers. Figure 6 shows a typical microprocessor-controlled flyback photoflash capacitor charger. Due to cost and microprocessor limitations, no sensing of primary current is done. In this case, only the output voltage is sensed in order to halt charging at the appropriate time. The microprocessor must control the gate of the NFET with appropriate ON and OFF times. The OFF times must be large enough so that the current in the primary of the transformer always stays in control. Since no direct sensing of the current is used, the OFF time must be conservative so that the flux in the transformer is always reset to zero each cycle. Thus, the flyback converter is operated heavily in the discontinuous mode region. This has several unwelcome consequences, including high peak currents in the primary of the transformer and the discrete NFET. The high peak currents are difficult to filter out and cause volt-

continued on page 16

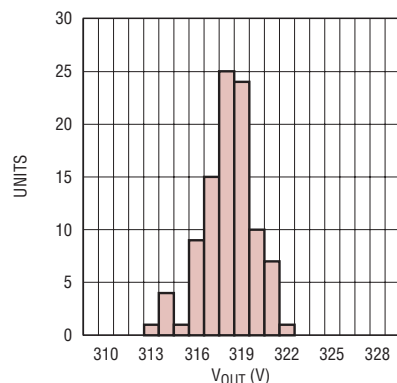


Figure 5. Output voltage histogram of ~100 LT3468 prototype boards.

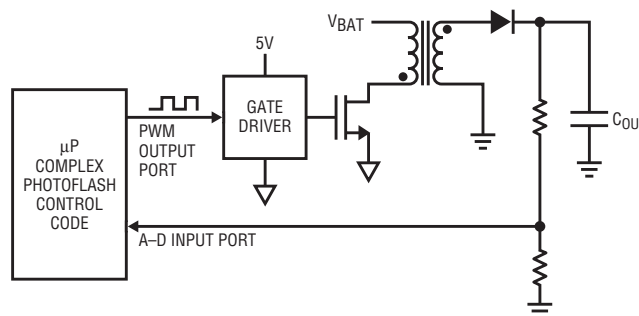


Figure 6. Typical microprocessor-controlled flyback photoflash capacitor charger. Due to cost and microprocessor limitations, no sensing of primary current is done—only the output voltage is sensed in order to halt charging at the appropriate time.

tion before the reset line falls. In our 5V example, using the 1.5% accurate supervisor, the system ICs must work down to 4.35V. System ICs working with a sloppier $\pm 2.5\%$ accurate supervisor must operate down to 4.25V, increasing the required system voltage margin, and the likelihood of system malfunction.

Noise Sensitivity

In any supervisory application, supply noise riding on the monitored DC voltage can cause spurious resets, particularly when the monitored voltage approaches the reset threshold. One common mitigation technique is to add hysteresis to the input comparator, but this has drawbacks. The amount of added hysteresis, usually specified as a percentage of the trip threshold, effectively degrades the advertised accuracy of the part. The LTC2903 does not use hysteresis.

To minimize spurious resets while maintaining threshold accuracy, the LTC2903 employs two forms of noise filtering. The first line of defense incorporates proprietary tailoring of the comparator transient response. Transient events receive electronic integration in the comparator and must exceed a certain magnitude and duration to cause the comparator to switch.

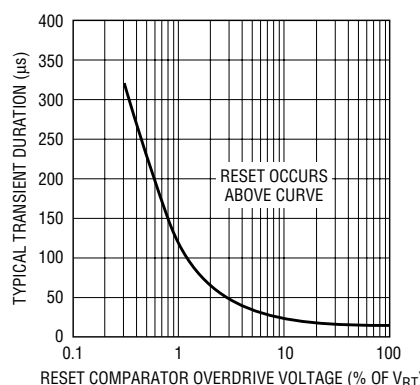



Figure 8. Typical transient duration vs overdrive required to trip comparator

Figure 8 illustrates the typical transient duration versus comparator overdrive (as a percentage of the trip threshold) required to trip the comparators. Once any comparator is switched, the reset line pulls low. The reset time-out counter starts once all inputs return above threshold, and the nominal reset delay time is 200 milliseconds. The counter clears whenever any input drops back below its threshold. This reset delay time effectively provides further filtering of the voltage inputs and is the second line of defense against noise. A noisy input with frequency components of sufficient magnitude above $f = 1/t_{RST} = 5\text{Hz}$ holds the reset line low, preventing oscillatory behavior on the reset line.

A reset line holding low provides a remarkably good indication of power supply problems. Common supply problems include improperly set output voltage and/or poor supply regulation.

Although all four comparators have built-in glitch filtering, use a bypass capacitor on the V1 and V2 inputs because the greater of V1 or V2 provides the V_{CC} for the part (a $0.1\mu F$ ceramic capacitor satisfies most applications). Apply filter capacitors on the V3 and V4 inputs if supply noise overcomes the built in filtering.

Conclusion

The LTC2903 quad supply monitor greatly improves system reliability by eliminating false resets and maintaining very high accuracy. Its proprietary reset pull-down circuit solves the long standing low voltage POR problem. The reset output can now maintain a logic-low at power-supply voltages down to zero volts. The reset output is guaranteed to sink at least $5\mu A$ ($V_{OL} = 0.15V$) for V1, V2 or V3 down to 0.5V. The LTC2903 monitors four voltages with 1.5% accuracy (over the entire temperature range) using comparators with built-in noise rejection. Non-standard voltages can be monitored with the 0.5V threshold adjustable input. 

LT3468, continued from page 6

age dips on the supply powering the converter. In the end, the efficiency of the converter suffers which leads to longer charge times.


To illustrate this, two mid-range digital cameras from an industry-leading company are analyzed. Both camera photoflash units use a microprocessor controlled flyback converter. The first microprocessor controlled circuit is simple while the second uses numerous external components to implement a more complex control scheme. Table 3a shows a comparison of the performance parameters between the LT3468 circuit and the microprocessor-based circuits. More telling, though, is Table 3b, which

makes the same comparison, but normalizes the input current.

The performance benefits of the LT3468 are obvious as shown in the nearly 44% reduction in charge time when compared to the microprocessor-based solutions. In addition to the charge time reduction, the LT3468 solution requires fewer, and smaller, components thus significantly reducing the overall size of the circuit.

Conclusion

The LT3468 and LT3468-1 provide a simple and efficient means to charge photoflash capacitors. The high levels of integration inside the parts result in tight output voltage distributions,

small solution size, lower total solution cost and minimal microprocessor software overhead. When compared to traditional methods, charge times can be lowered by more than 44%. The LT3468 family offers a range of input currents for flexibility in the trade-off between input current and charge time. 

for
the latest information
on LTC products,
visit
www.linear.com