

by Wei Chen

## Introduction


The LTC1709-8/LTC1709-9 are dual, current mode, PolyPhase™ controllers that drive two synchronous buck stages out of phase. This architecture reduces the number of input and output capacitors without increasing the switching frequency. The relatively low switching frequency and integrated high current MOSFET drivers help provide high power-conversion efficiency for low voltage, high current applications. Because of the output ripple current cancellation, lower value inductors can be

used, resulting in a faster load transient response. This, plus the 5-bit VID table, makes these devices particularly attractive for CPU power supply applications. Two VID tables are available to comply with the VRM 8.4 (LTC1709-8) and VRM9.0 (LTC1709-9) specifications.

## Design Example

Figure 1 shows the schematic diagram of a 42A power supply for the AMD Athlon microprocessor. With only one IC, eight tiny SO-8 MOS-

FETs and two  $1\mu\text{H}$  low profile, surface mount inductors, an efficiency of 86% is achieved for a 5V input and a 1.6V/42A output. Greater than 85% efficiency can be maintained throughout the load range of 3A–42A, as shown in Figure 2. Because of the low input voltage, the reverse recovery losses in the body diodes of the bottom MOSFETs are not significant. No Schottky diodes are required in parallel with the bottom MOSFETs in this application.

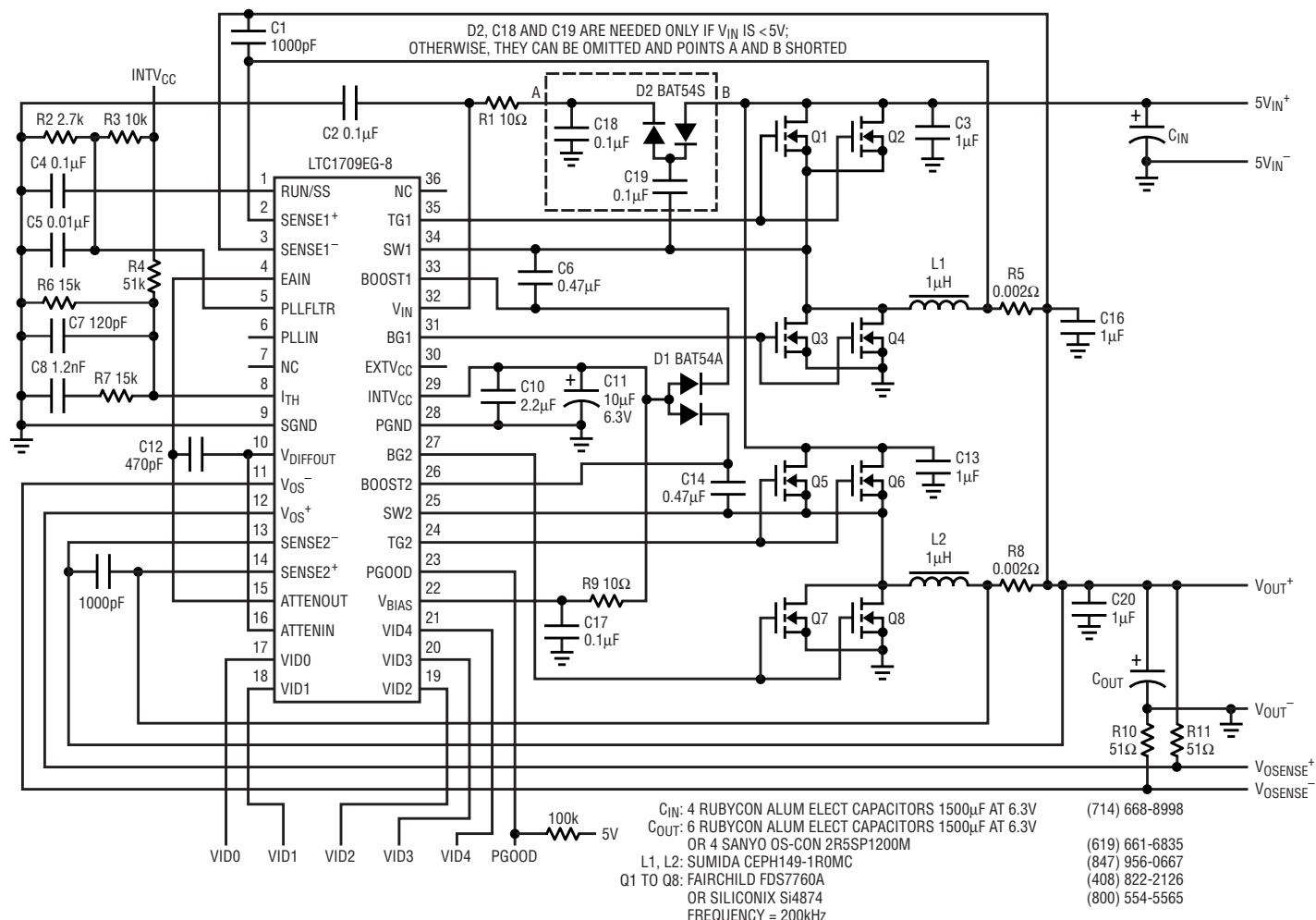

**Figure 1. Schematic diagram of a 42A power supply using the LTC1709**


**Table 1. Comparison of input and output ripple current for single-phase and dual-phase configurations ( $L = 1\mu\text{H}$ ,  $f_s = 200\text{kHz}$ )**

Phases	Input Ripple Current ( $A_{RMS}$ )	Output Ripple Current ( $A_{P-P}$ )
1	19.7	10.9 <sup>1</sup>
2	10.1	2.9

<sup>1</sup>Assumes that the single-phase circuit uses two  $1.0\mu\text{H}/21\text{A}$  inductors in parallel to provide 42A output.


Table 1 compares the input and output ripple currents for single-phase and 2-phase configurations. A 2-phase converter reduces the input ripple current by 50% and the output ripple current by 75% compared to a single-phase design. The reduction in the cost and size of the input and output capacitors is significant.

Figure 3 shows the measured load transient waveform. The load current changes between 2A and 42A with a slew rate of about  $30\text{A}/\mu\text{s}$ . Output capacitor type and size requirements are dominated by the total ESR of the output capacitor network. Six low cost aluminum electrolytic caps (Rubycon,  $1500\mu\text{F}/6.3\text{V}$ ) are needed on the

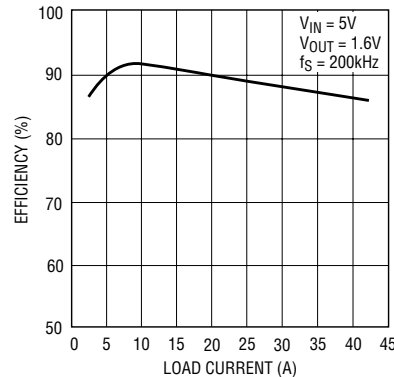

**Figure 2. Efficiency vs load current for Figure 1's circuit**

output to meet this requirement. The maximum output voltage variations during the load transients are less than  $200\text{mV}_{P-P}$ . Active voltage positioning was employed in this design to keep the number of output capacitors at six (refer to Linear Technology Design Solutions 10 for more details on active voltage positioning). R4 and R6 provide the output voltage positioning with no loss of efficiency. If OSCON caps are used, four  $1200\mu\text{F}/2.5\text{V}$  (2R51200M) capacitors will be sufficient.

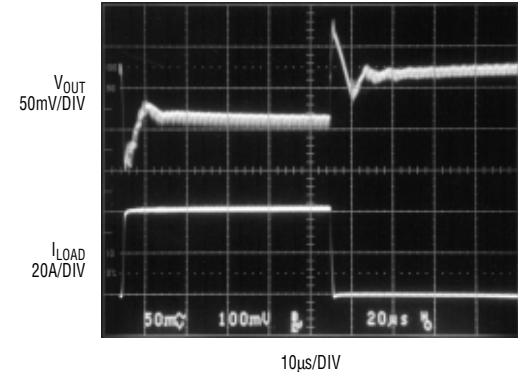

**Figure 3. Load transient waveforms at 40A step and  $30\text{A}/\mu\text{s}$  slew rate**

## Conclusion

The LTC1709 based, low voltage, high current power supply described above achieves high efficiency and small size simultaneously. The savings in the input and output capacitors, inductors and heat sinks help minimize the cost of the overall power supply. This LTC1709 circuit, with a few modifications, is also suitable for VRM9.0 applications. Refer to Linear Technology Application Note 77 for more information on the PolyPhase technique. 