

## IN THIS ISSUE...

### COVER ARTICLE

**Complete USB Power Manager, Li-Ion Charger and Two Buck Converters in a 4mm x 4mm QFN** ..... 1  
Bryan Legates

**Issue Highlights** ..... 2

**LTC in the News**..... 2

### DESIGN FEATURES

**Easy-to-Use Spread Spectrum Clock Generator Reduces EMI and More ..** 6  
Tim Regan and Doug La Porte

**Monolithic Ideal Diode Prolongs Battery Life**..... 10  
Andrew Bishop

**Versatile Power Supply Tracking without MOSFETs**..... 13  
Dan Eddleman

**Compact, Versatile, Accurate, 3-State Programmable Power Supply Supervisors**..... 19  
Eko T. Lisuwandi

**2-Phase Controller Makes Small, Fast and Efficient Power Supplies with Output Tracking**..... 24  
David Chen

### DESIGN IDEAS

..... 27-36  
(complete list on page 27)

**New Device Cameos**..... 37

**Design Tools** ..... 39

**Sales Offices**..... 40

# Complete USB Power Manager, Li-Ion Charger and Two Buck Converters in a 4mm x 4mm QFN

## Introduction

The LTC<sup>®</sup>3455 provides a compact, easy-to-use solution that seamlessly transitions between three different input power sources: a single-cell Li-Ion battery, a USB port, and a 5V wall adapter. The device contains two synchronous buck (step-down) DC/DC converters, a USB power controller (that accurately limits USB current to 500mA or 100mA), a full-featured single-cell Li-Ion battery charger, a 200mA Hot Swap<sup>™</sup> output, a low-battery indicator, and numerous internal protection features, all squeezed into a low-profile (0.8mm tall) 4mm x 4mm 24-Pin QFN package (Figure 1).

The simplicity of a typical LTC3455 application is shown in Figure 2. Efficiencies for the DC/DC converters in this application are shown in Figure 3. The device handles important system startup and protection issues internally (soft-start, supply sequencing,

by Bryan Legates

charger thermal limiting, current limiting for all outputs, etc.) which helps minimize the number of external components. The circuit is even simpler for applications that require only a battery and USB power, without the 5V wall adapter (see note in Figure 2).

## Dual High-Efficiency DC/DC Converters

The LTC3455 contains two 1.5MHz constant-frequency current-mode switching regulators that operate with efficiencies up to 96%. Switcher 1 provides up to 400mA at 1.5V/1.8V (to power a microcontroller core), and Switcher 2 provides up to 600mA at 3.3V (to power microcontroller I/O, memory and other logic circuitry). Both converters support 100% duty cycle operation (low dropout mode) when the input voltage drops very close to the output voltage, and both are capable

continued on page 3

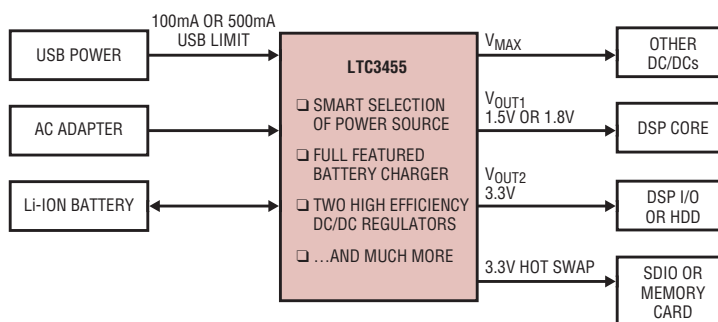


Figure 1. A complete "plug-and-play" portable power management solution in a tiny package

# Issue Highlights

Managing power in portable devices has never been easier. Our cover article introduces a device that distills all portable power management tasks into one easy-to-use 16mm<sup>2</sup> device.

The LTC3455 **Portable Device Power Manager** manages power from three sources, including current-limited USB, wall adapter, and Li-Ion battery, charges the battery, supplies two DC outputs, and offers Hot Swap support for memory cards—all with just a few external components.

In some applications the LTC3455 can replace a fistful of power management and power conversion devices.

## Featured Devices

Below is a summary of the other devices featured in this issue.

### Programmable SSFM Oscillator

One effective method to reduce switcher-based power supply EMI at a particular frequency is to spread the EMI energy amongst many frequencies. To this end, a switcher's operating frequency can be modulated via Spread Spectrum Frequency Modulation (**SSFM**). The LTC6902 is an easy-to-use **resistor programmable clock generator** that outputs a pseudo-random clock signal. This clock signal can be applied to a switching regulator to implement SSFM.

The LTC6902 can also be used to reduce aliasing in ADCs (discussed in the article herein). (Page 6)

### PowerPath Control

Many consumer electronic devices rely on batteries and wall adapters for supplying power to portable and handheld applications. These devices must rely on some method of automatically and smoothly switching between the battery and the wall adapter.

The LTC4411 is a **low loss monolithic ideal diode** that simplifies the implementation of PowerPath™ control circuitry. With the LTC4411 it is possible to build an entire power management solution in a 2mm×3mm footprint. (Page 10)

### Supply Sequencing and Tracking

The LTC2923 provides a simple and versatile solution to both **power supply tracking and sequencing** without the drawbacks of series MOSFETs.

By selecting a few resistors, the supplies are configured to ramp-up and ramp-down with a variety of voltage profiles. The data sheet for this part presents a simple 3-step design procedure for choosing the resistor values.

The article here presents some of the theory behind the 3-step procedure for users who want a more intuitive understanding of the operation of the part. (Page 13)

### Power Supply Monitoring

Four new power supply supervisors improve system reliability by offering very accurate reset thresholds. They save design time, production costs and board space with simple interfaces and extremely low part count.

The LTC2904, LTC2905, LTC2906 and LTC2907 dual **power supply supervisors** can simultaneously monitor two supply voltages with 1.5% threshold accuracy over temperature. All four parts can be programmed to have either a 5%, 7.5% or 10% power supply tolerance. (Page 19)


### Power Supply Regulators and Controllers

High efficiency, small size and fast transient response are often at odds in power supply designs. The LTC3708 **dual, 2-phase PWM step-down DC/DC controller** makes it possible to simultaneously achieve all three by offering a unique set of powerful features.

The LTC3708 uses a constant on-time, valley-current control architecture to regulate each output independently. The on-time of the first output channel is programmed by an external resistor so that the switching frequency is kept relatively constant. An internal Phase Locked Loop (PLL) locks the frequency of the second output channel to that

## LTC in the News...

On January 13, Linear Technology Corporation announced its financial results for its second quarter of fiscal year 2004, ending December 28, 2003. According to Robert H. Swanson, Chairman of the Board and CEO, "This was a strong quarter for us. We exceeded our estimates by growing sales and profits 7% sequentially over the September quarter. Demand for our products was particularly strong and increased in each end-market, led by industrial and communications. This broad cross section of strength, which crosses all end-markets and all major geographies, and is widely disbursed over many customers, is very encouraging. We continue to be both strongly profitable, as demonstrated by our 40% return on sales, and strongly cash flow positive from operations, as evidenced by the increase in cash. Looking forward we envision continued strength in our marketplace. Should these current trends continue, we expect to grow both sales and profits in the high single digit range sequentially in the March quarter."

The Company reported net sales for the quarter of \$186,021,000 and net income of \$74,335,000. Diluted earnings were \$0.23 per share. A cash dividend of \$.08 per share, an increase of \$.02 per share, will be paid on February 11, 2004 to stockholders of record on January 23, 2004. 

of the first channel but with a 180° phase shift—this 2-phase operation reduces the input RMS current and EMI. (Page 24)

## Design Ideas and Cameos

Starting on page 27 are seven new Design Ideas, and at the back are eight New Device Cameos. Visit [www.linear.com](http://www.linear.com) for complete device specifications and applications information. 

LTC3455, continued from page 1

of Burst Mode® operation for highest efficiencies at light loads (Burst Mode is pin selectable). Switcher 2 has independent ON/OFF control, but operates only when Switcher 1 is also enabled and in regulation. If both are enabled at initial power-up, Switcher 2 turns on only after Switcher 1 has reached 90% of its programmed value. This power-up delay ensures proper supply sequencing and reduces the peak battery current at startup.

Whenever external power is present, the battery charger and Switcher 1 (the core supply) are enabled. This ensures that the battery can always be charged and that the microcontroller is always alive whenever external power is available. Switcher 2 can also be set to turn on whenever external power is present. Additionally, all system power is drawn from the appropriate external source, and once the battery is fully charged, current drain on the battery is reduced to 10µA.

## Make the most of USB Power

The popularity of USB (Universal Serial Bus) makes it an attractive choice for transferring data and power between devices. The ability to power a portable device via USB while charging its batteries is obviously desirable (no wall wart), but it is not necessarily an easy design problem. The power available from a single USB port (maximum 2.5W) is barely enough to support the peak power needed by many full-featured portable devices, even without adding in the power needed to quickly charge their batteries.

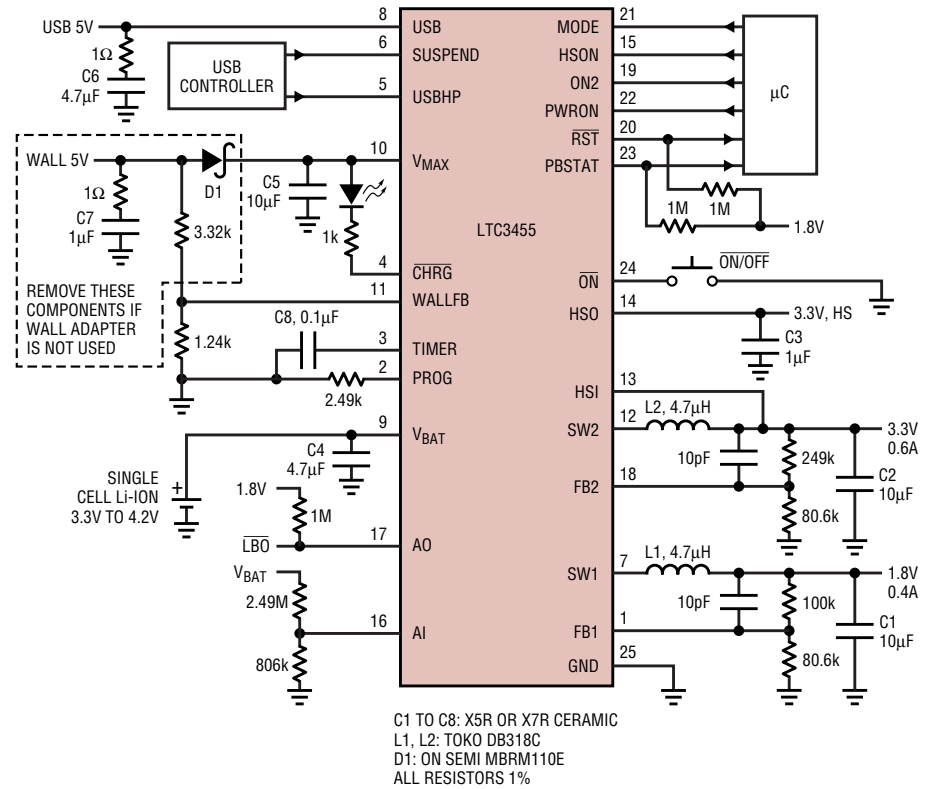


Figure 2. Typical LTC3455 application

To further complicate matters, the USB port is not an ideal power source. Each device can draw a maximum of 500mA in high power mode (or 100mA in low power mode), but the voltage provided to the portable device can vary quite significantly. Although the USB power supply has a 5V nominal rating, when you include normal supply variations, cable losses, and transient conditions, the USB voltage showing up at the portable device is typically much lower—often falling to only 4V (even though the minimum USB specification is 4.35V). Since the USB port has a strict current limit of 500mA,

this means the amount of power available to the portable device can be as low as 2W. The reduced USB voltage also presents problems when trying to fully charge a single-cell Lithium-Ion battery (that has a 4.2V final charge voltage) when the USB voltage may itself be below 4.2V.

The LTC3455's USB power controller is specifically designed to solve these problems by offering several features that make the most of the power the USB port has to offer. The device draws USB power once the USB pin voltage reaches 3.9V, and continues drawing power until the

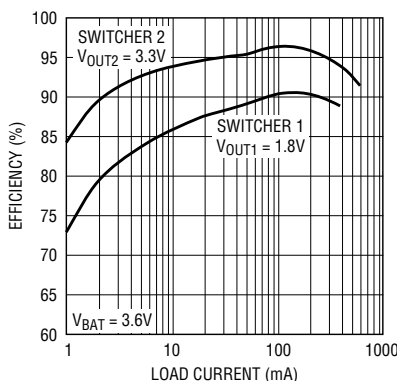


Figure 3. DC/DC converter efficiencies

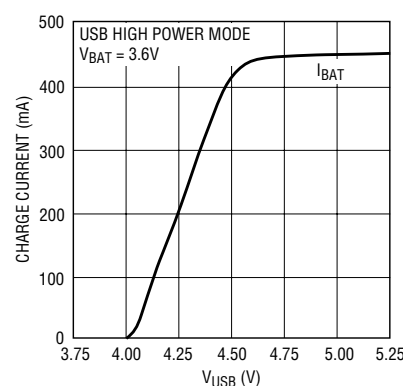


Figure 4. Charge current vs USB voltage

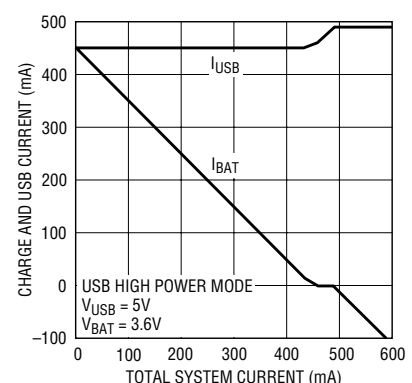


Figure 5.  $I_{BAT}$  vs total system current



pin voltage falls below 3.7V. If the USB pin voltage drops below 4.5V, the charge current gradually reduces (and eventually shuts off around 4.0V) to help prevent “chattering” and stability problems when using long, resistive USB cables. Figure 4 shows this reduction in charge current as USB voltage drops.

The internal USB power controller also automatically throttles back the battery charge current to help keep the total system current under the strict 500mA or 100mA USB limit. The rest of the system draws whatever current it needs, but the battery charge current is reduced to try and keep the total system current below the strict USB 500mA/100mA limit. The graph in Figure 5 shows how charge current,  $I_{BAT}$ , decreases as the current needed for the rest of the system increases (both switchers and all other external devices pull current from the  $V_{MAX}$  pin). The total USB current,  $I_{USB}$ , always stays below 500mA.

## Li-Ion Battery Charger

The battery charger is a constant-current, constant-voltage charger. In constant-current mode, the maximum charge current is set by a single external resistor. When the battery approaches the final float voltage, the charge current begins to decrease as the charger switches to constant-voltage mode. The charge cycle is terminated only by the charge timer, which is programmed using a single external capacitor. Maximum charge current is 500mA when USB powered and up to 1A when wall adapter powered. The USB power controller will automatically throttle back the charge current to help keep the total USB pin current below 500mA whenever under USB power. When the battery is below 2.8V at the start of a charge cycle, the charger goes into trickle charge mode, reducing the charge current to one-tenth of its programmed maximum value. An internal thermal limit reduces the charge current if the die temperature rises above a preset value of approximately 105°C. This feature not only protects the LTC3455 from excessive temperatures, it can also re-

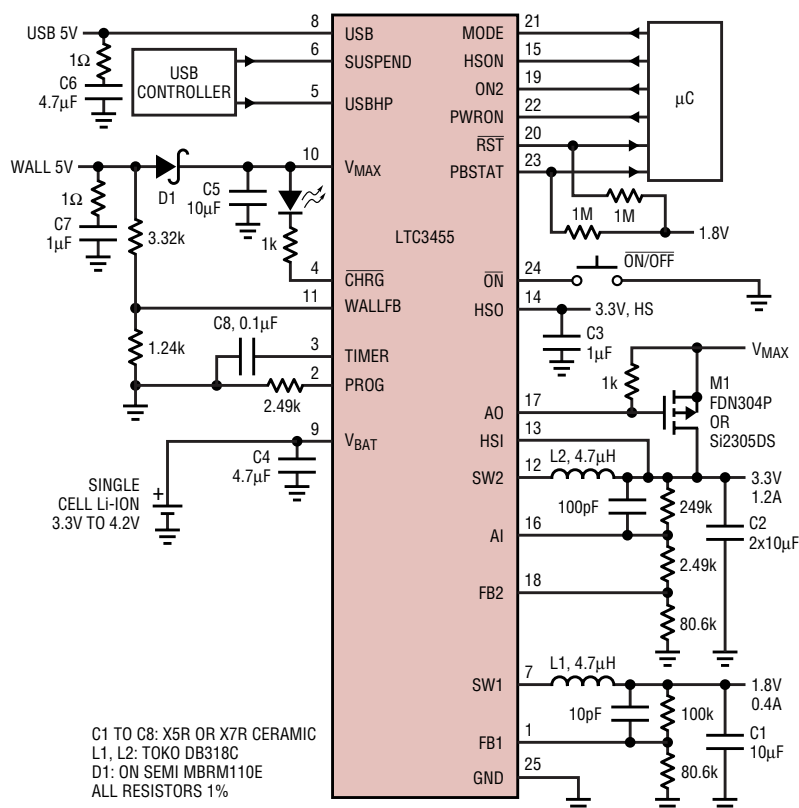


Figure 6. LTC3455 application with 3.3V output current increased to 1.2A

duce charge times because it allows the user to set a higher maximum charge current—taking into account *typical*, instead of worse case, ambient temperatures for a given application—with the assurance that the charger will automatically reduce the current under worst-case conditions.

## Hot Swap Output

A 200mA Hot Swap output is provided for powering Secure Digital (SDIO) cards, memory cards, and any other external devices that can be hot-plugged into the system. If hot-plugged directly into one of the switcher outputs, these external devices appear initially as a short and can drag down the output, causing major

system problems. The HSO output can only operate when the LTC3455 is on, and is enabled using the HSON pin. For applications where hot-plugging is not needed, this output can simply be used as a 200mA load switch (controlled by the HSON pin).

## Low Battery Detector/LDO

The LTC3455 contains an additional gain block (pins AI and AO) that can be used as either a low-battery indicator, or as an LDO with the addition of an external PNP or PMOS. This gain block is alive whenever the device is enabled, and turned off during shut-down to minimize battery drain. The low-battery detector will not report a low-battery condition until the

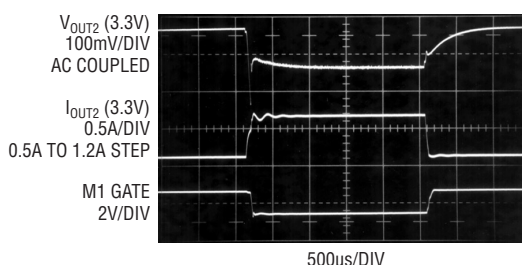


Figure 7. Load current step (0.5A to 1.2A) for 3.3V output

LTC3455 is turned on, but this is not a problem for most applications, since the LTC3455 would power the microcontroller and all other intelligence in the system anyway. The LDO is convenient for applications needing a third output, like a 2.5V or a quiet 3V supply.


## Increasing the 3.3V Output Current to 1.2A

With an internal current limit of 900mA, Switcher 2 typically provides a 3.3V, 600mA output. While this output current is sufficient for many portable devices, some applications need a 3.3V supply capable of providing more than 1A. Figure 6 shows how to implement a higher current 3.3V output using the LTC3455. By adding one tiny SOT-23 PMOS and using the gain block as an LDO, the 3.3V output now provides 1.2A of output current. Switcher 2 is programmed for an output voltage of 3.3V, and the LDO is programmed for an output voltage of 3.2V (3% lower). As long as the load current is low enough for Switcher 2 to provide, the LDO is turned off completely. This circuit is ideal for applications that need the higher 3.3V output current for only a brief time. Switcher 2 will normally provide all of the output current, and the LDO will turn on briefly to provide the higher load currents.

When the load current exceeds what Switcher 2 can provide, the 3.3V output droops slightly and the LDO provides the additional current needed. Figure 7 shows the transient response when the 3.3V output current is stepped from 0.5A to 1.2A. More output capacitance can be added to improve the 3.3V transient response during these high current load steps.

## USB Power Supply with Temporary Backup Power

Although designed primarily for Li-Ion powered portable applications, the LTC3455 is also a good choice for systems that are always powered by a USB supply or wall adapter. The battery charger can then be used to charge up a large capacitor or backup battery, which briefly provides power

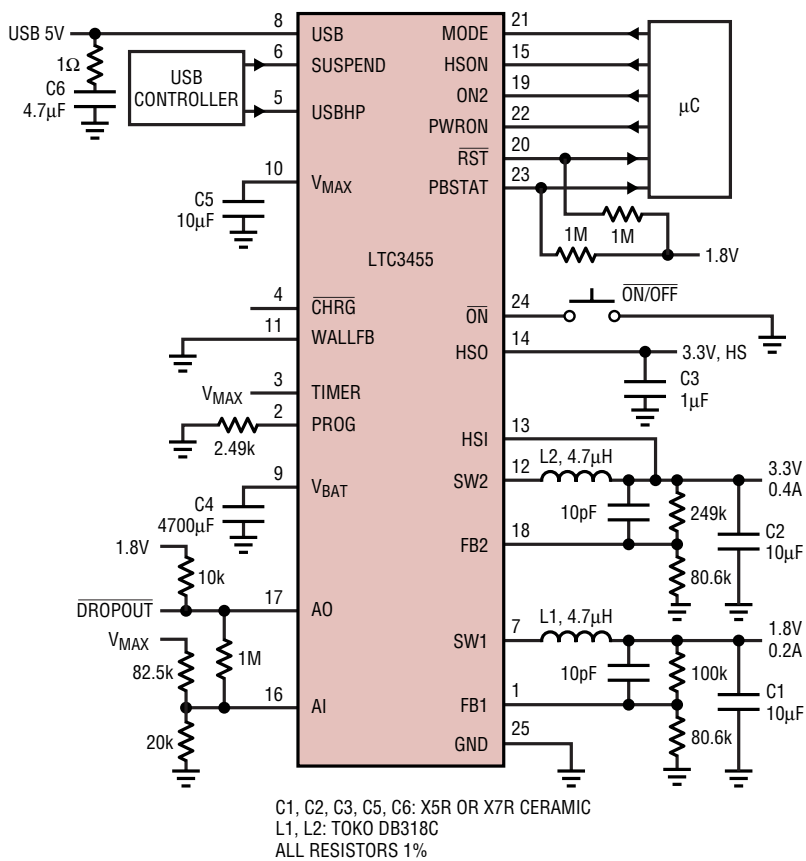

**Figure 8. Standalone USB power supply with temporary backup power**

to the system after the external power has been removed. This gives the microcontroller enough time to follow proper shutdown procedures when the main power source is abruptly removed.

Figure 8 shows a standalone power supply for USB high power applications (500mA max USB current) using the LTC3455. The total system power should be kept below 1.8W to ensure clean operation even under worst-case USB conditions. With the resistor values shown, the low-battery indicator (AI and AO pins) triggers when the  $V_{MAX}$  pin voltage drops to 4.0V, notifying the microcontroller of an impending dropout condition. The 1M $\Omega$  resistor connected between the AI and AO pins provides 150mV of hysteresis (the dropout indicator stays low until the  $V_{MAX}$  pin rises back above 4.15V).

A 4700 $\mu$ F backup capacitor connected to the V<sub>BAT</sub> pin briefly provides power to the system after the USB supply has been removed, and also helps support transient loads that slightly exceed the USB current limit. Connect-

ing this large capacitance to the  $V_{BAT}$  pin has several advantages. It provides a large energy reservoir that is isolated from both the USB pin (the USB specification limits capacitance on the USB supply pin to 10 $\mu$ F or less) and the  $V_{MAX}$  pin (using a very large capacitance on this pin will delay the system turn-on), and it prevents large inrush currents by using the battery charger to slowly charge this capacitor. With the **TIMER** pin tied to  $V_{MAX}$ , the battery charger operates in constant-current mode (the voltage-loop and timer function are disabled), so the 4700 $\mu$ F capacitor is always fully charged to the available USB voltage.

## Conclusion

The LTC3455 simplifies the design of portable applications. It is a complete power management solution, incorporating two step-down DC/DC converters, a USB power controller, a full-featured Li-Ion battery charger, a Hot Swap output, and a low-battery indicator—all squeezed into a tiny 4mm × 4mm QFN. 