 


**Figure 3. Measured efficiencies of Stage Shedding operation and conventional operation for the VRM9 design**

current sharing, even if the layout of parallel power stages is not symmetrical;

- All controllers feature integrated high current MOSFET drivers for up to 600kHz switching frequency, thus minimizing the overall power supply size and component count.

LTC3731 is a versatile 3-phase controller that generates a 30 or 60 degree clock output based on the voltage level of the PHASMD pin. This feature allows several LTC3731s to be paralleled for up to 12-phase operation. The 0.6V to 6V output voltage is programmed by an external resistor divider. The LTC3730 is a dedicated 3-phase controller with 5-bit VID output programming that



**Figure 4. Load transient waveforms for the VRM9.1 design**

is compatible with IMVP2 and IMVP3 requirements. The internal op amp can be used to program voltage offsets for different CPU operation modes. This controller is suitable for powering Intel mobile Northwood CPUs. The LTC3732 is another 3-phase controller with a 5-bit VID output programming that is compatible with VRM9.x specs. This controller is suitable for powering Intel desktop Pentium 4 (P4) CPUs in a so called DeskNote PC or Transportable PC design. A DeskNote PC uses the desktop CPU in a notebook computer design to simultaneously achieve high performance and low cost. All three controllers are available in space saving SSOP36 packages, while the LTC3731 is also available in the much smaller, and thermally enhanced, 5mm × 5mm QFN package.

## Stage Shedding Operation Improves Efficiency at Light Loads


There are three main obstacles to obtaining high efficiency at light loads with a PolyPhase converter:

- Switching related losses
- Extra conduction losses induced by circulating currents
- IC bias losses


The first two obstacles, described below, are reduced by the Stage Shedding feature. The IC bias losses can be reduced by enabling Burst Mode® operation.

## Light Load Efficiency Obstacle 1: Switching-Related Power Losses

In high current applications, low  $R_{DS(ON)}$  MOSFETs are typically chosen to minimize conduction losses at full loads. At light loads, though, the high gate charge and parasitic capacitance of these MOSFETs often cause significant power losses associated with gate driving and switching. Also, the core losses of inductors dominate the overall inductor power losses at light loads. Since the switching losses, gate driving losses, and inductor core losses do not decrease with load currents, light load efficiency suffers.

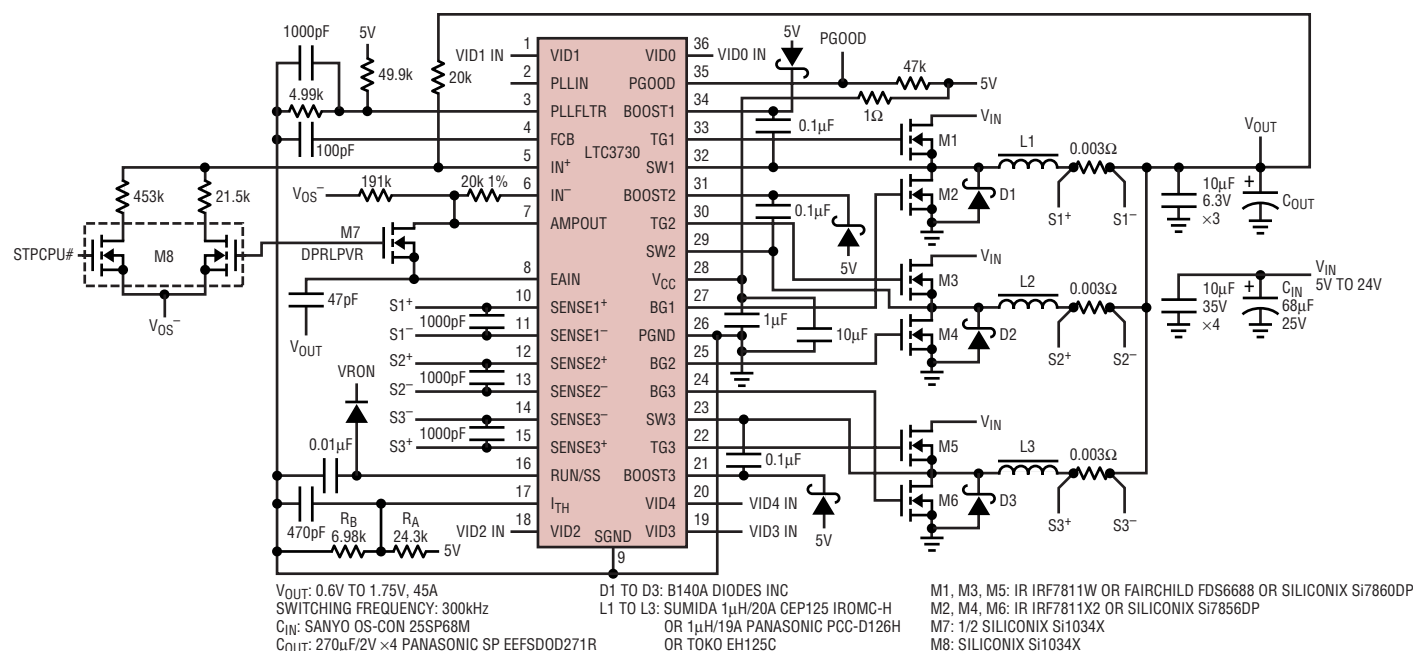

**Figure 5. IMVP3 compatible, 45A, 3-phase power supply**

 

### Light Load Efficiency Obstacle 2: Circulating Currents

In a PolyPhase synchronous buck converter, the inductor current in each synchronous buck stage is allowed to reverse at light loads due to synchronous rectification. In a practical PolyPhase design, a current sharing error always exists because of tolerances in the sense resistors and slight mismatches between paralleled channels within the controllers. Any current sharing error among the paralleled stages introduces circulating currents that result in additional power losses. As shown in Figure 1, for example, if the current difference between two paralleled channels is 2A ( $I_{ER}=1A$ ), one channel (Channel 1) will source 1A and the other channel (Channel 2) will sink 1A at no load conditions. Since this 1A current circulates between two channels instead of flowing toward the output, this current introduces unnecessary power losses. Therefore, the circulating current must be minimized to improve light load efficiency in a PolyPhase converter.

### The Solution: Stage Shedding Operation

A simple solution is to turn off the bottom FET when the inductor current starts to reverse. This is called pulse skipping in most LTC controllers. This scheme significantly reduces the reverse current. However, an accurate detection of inductor current zero-cross and an immediate turn-off of the bottom FETs are difficult to achieve. A more effective scheme, as implemented in new 3-phase controllers,

is the Stage Shedding technique. At light loads, the controllers automatically shut down all but one channel. This scheme completely eliminates the circulating currents and related power losses. Furthermore, Stage Shedding eliminates the gate drive losses, MOSFET switching losses, and inductor core losses of the unused channels. Thus the Stage Shedding technique decreases the conduction losses and switching losses significantly at light loads, resulting in a much higher efficiency at light loads. Since the controller maintains the original regulation loop, Stage Shedding has no effect on output regulation accuracy.

### Burst Mode Operation Minimizes Obstacle 3: IC Bias Losses

To further minimize the IC bias losses and switching losses at no load condi-

tions, Burst Mode operation can be enabled by applying a voltage between 0.6V and ( $V_{CC} - 1V$ ) to the FCB pin.

### 3-Phase, High Efficiency 65A VRM9.x Power Supply for Pentium® 4 CPU

Figure 2 shows a 3-phase VRM9.x power supply for a Pentium® 4 CPU. It uses the LTC3732 to drive nine small PowerPak SO-8 MOSFETs for 65A output current. To provide higher output currents, simply use lower  $R_{DS(ON)}$  MOSFETs and higher current rated inductors.  $R_A$  and  $R_B$  implement a lossless active voltage positioning (AVP) technique to minimize the output capacitor size. For more detailed technical information about AVP see the LTC1736 data sheet or Design Solution 224. Figure 3 shows the measured efficiency under different load conditions. In this case the input is 12V, the output voltage is 1.5V and the switching frequency is 220kHz. The efficiencies are measured for both Stage Shedding operation and for conventional PolyPhase operation (with all channels ON). As the chart shows, Stage Shedding operation significantly improves efficiencies at light loads ( $\leq 10A$ ). At 1% of full load (0.6A), Stage Shedding operation improves efficiency more than 25%. Figure 4 shows the load transient response waveform for the 30A load step. With ten POSCAPS (330 $\mu$ F/2.5V,

Pentium is a registered trademark of Intel Corporation

 


Figure 7a. 6-phase configuration


 


Figure 7b. 12-phase configuration

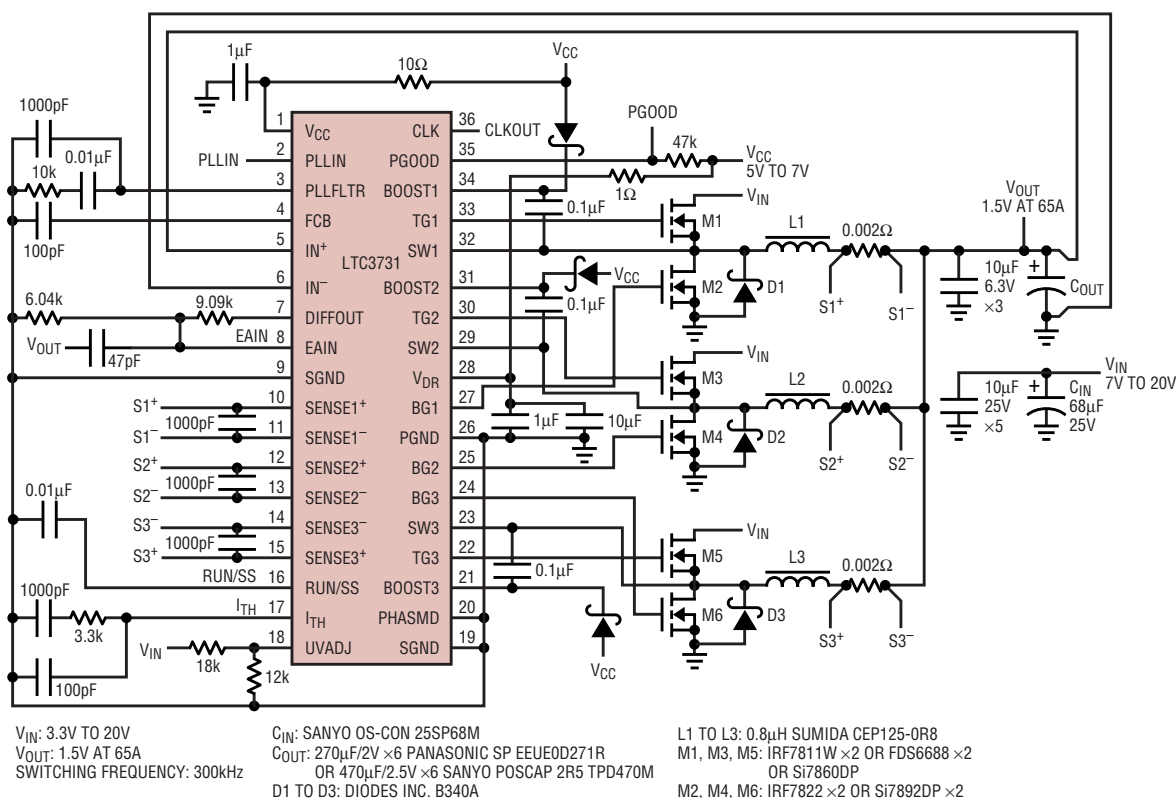

**Figure 8. Basic 3-phase block using the LTC3731**

12mΩ ESR) at the output, the output voltage variation is about 70mV<sub>P-P</sub>. The AVP loadline slope is 0.9mΩ in this design.

### 3-Phase IMVP3 Compatible Power Supply for Mobile Northwood CPUs

Figure 5 shows an IMVP3 power supply for a mobile Northwood CPU. It uses the LTC3730 to drive six small PowerPak SO-8 MOSFETs for up to 45A output current. Like in the previous example,  $R_A$  and  $R_B$  implement the AVP to minimize the output capacitor size. The IMVP3 specs also require three digital signals in addition to the 5 VID bits to set the output voltage under different operational modes: battery optimized mode (BOM), performance optimized mode (POM), deep sleep mode (DPSLP), and deeper sleep mode (DRPSLPVR). Under the BOM, DPSLP and DRPSLPVR modes, the output voltage is reduced to conserve the battery energy.

Figure 6 shows the measured efficiency under performance mode and deeper sleep modes, where the input is 15V and the switching frequency is 250kHz. The efficiency in

performance mode exceeds 82% at 1.3V output over a load range of 3A to 45A. Efficiencies in deeper sleep mode were measured for both Stage Shedding operation and conventional PolyPhase operation. Stage Shedding operation improves the efficiencies significantly in deeper sleep mode: about 10% improvement at 5A current. This corresponds to a power loss saving of 0.7W. In a notebook application, the idle time represents about 70% of the run time, this power saving at deeper sleep mode can generate about 4% longer battery run time (assuming 53Whr battery and 4 hour battery run time).

### Versatile LTC3731 Powers Up to 200A Current with 12-Phase Operation

The LTC3731 has a CLKOUT pin that produces a 30 degree or 60 degree clock output (referenced to TG1 rising edge) based on the voltage level of the PHASMD pin. Therefore, multiple LTC3731s can be daisy-chained to produce a 6- or 12-phase operation. Since the error amplifier of the voltage

feedback loop is a  $g_m$  amplifier, the  $g_m$  amplifiers of the LTC3731s can be paralleled, creating a common error amplifier that has an equivalent gain of  $(g_m \cdot n)$ , where  $n$  is the number of LTC3731s in parallel. Figure 7 shows the block diagram for a 6-phase and a 12-phase circuit. Figure 8 shows the detailed schematic diagram of one of the 3-phase blocks shown in Figure 7. Each 3-phase block is capable of 65A load current.

### Conclusion

LTC3730, LTC3731 and LTC3732 based 3-phase power supplies can deliver high efficiency over a wide load range. Stage Shedding operation significantly improves efficiency at light loads, making this controller family particularly attractive for battery-powered applications where improved light load efficiency can increase battery run time. This family also includes features that make power supplies smaller and more robust, including overcurrent latchoff and overvoltage protection. 