

Figure 2. Tunable second order Butterworth lowpass response using the LTC6912-2

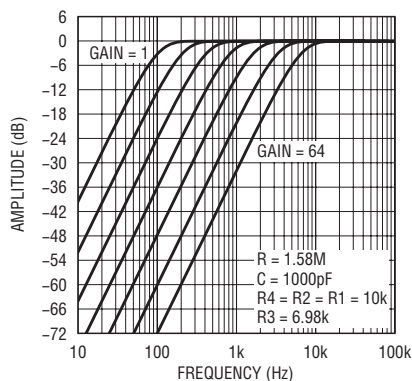


Figure 3. Tunable second order Butterworth highpass response using the LTC6912-2

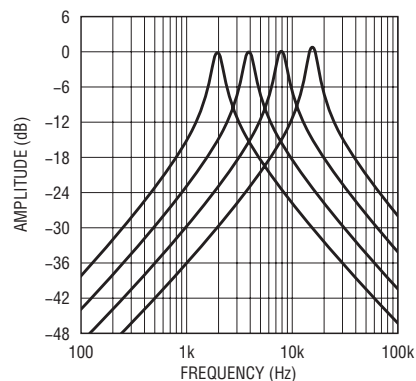


Figure 4. Tunable second order bandpass filter using an LTC6912-1 with gains 1–8

for a lowpass, bandpass and highpass filters respectively.

A Tunable Lowpass or Highpass Filter

The shape of the amplitude response of the second order depends on the f_0 frequency relative to the cutoff frequency and the Q value. In a second order Butterworth highpass or lowpass response the f_0 frequency is equal to f_{CUTOFF} ($f_{-3\text{dB}}$) and the filter's Q value is equal to 0.707. In a second order Bessel highpass or lowpass response

the f_0 frequency is equal to $1.274 \cdot f_{\text{CUTOFF}}$ and the filter's Q value is equal to 0.577. Figure 2 shows the tunable range of a Butterworth lowpass filter using an 100Hz integrator frequency ($R = 1.58\text{M}\Omega$, $\pm 1\%$ and $C = 1000\text{pF}$, $\pm 5\%$) and an LTC6912-2 to tuned the filter's f_{CUTOFF} from 100Hz to 6.4kHz. Figure 3 shows the tunable range of a Butterworth highpass filter that is the mirror oposite of the lowpass filter reponse of Figure 2. The output response to a step change is approximately equal to $5/f_{\text{CUTOFF}}$, (if the step

change is to a $1\text{kHz } f_{\text{CUTOFF}}$ then the filter settles five milli-seconds after a step change). The maximum tunable f_0 frequency is a function of the gain-bandwidth product of the op amps and the circuit's sensitivity to the highest PGA gain that is used for tuning. For the amplifiers shown, based on empirical data, a maximum f_0 of $800\text{kHz}/[Q \cdot \text{Gain}]$ limits gain error to $\leq 2\text{dB}$. For example, if only the lowest 1, 2, 5 and 10 gains of an LTC6912-1 are used for tuning, a second order Butterworth lowpass filter ($f_0 = f_{\text{CUTOFF}}$)

continued on page 45

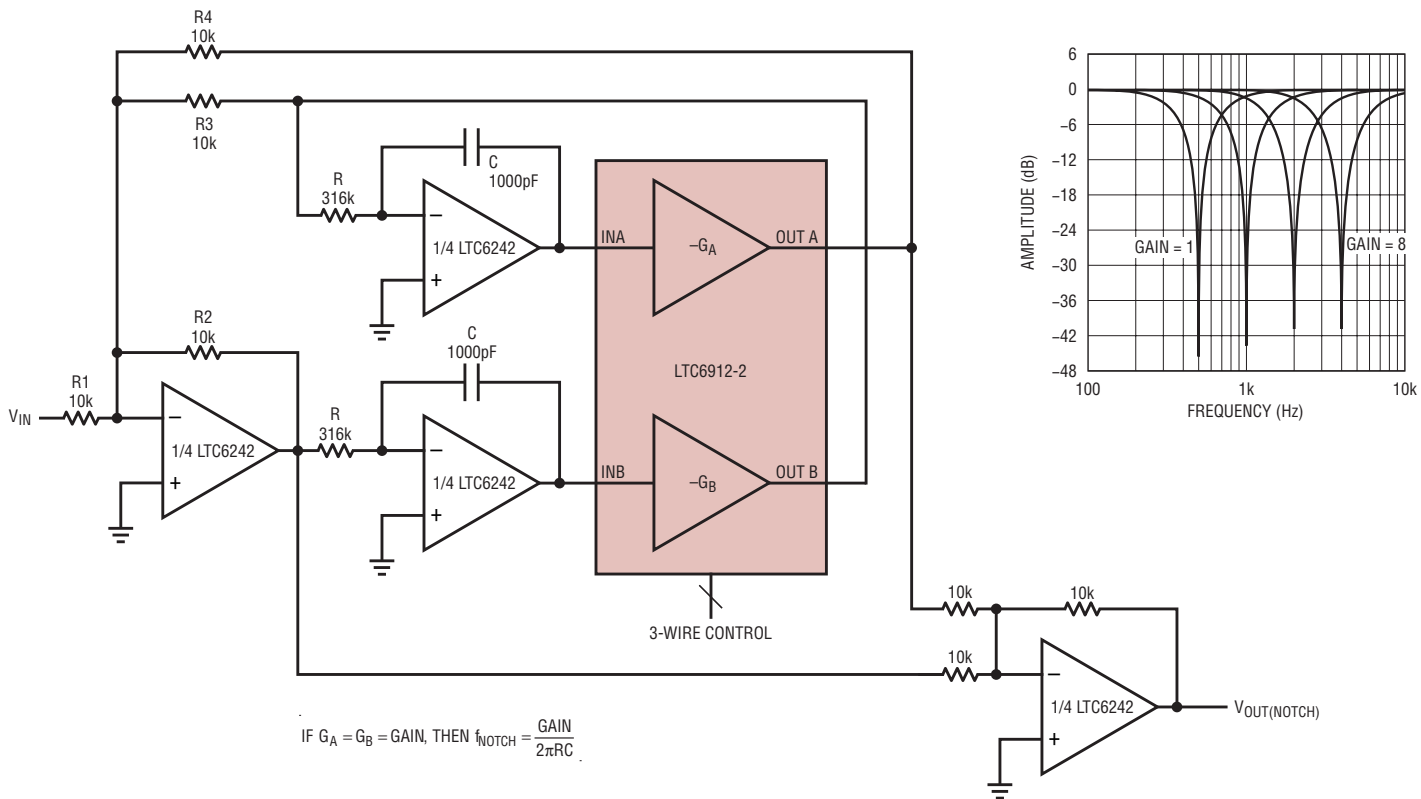


Figure 5. An SPI-tunable second order notch filter

P-channel MOSFET switch is turned on continuously, thereby maximizing the usable battery life.

A Power-On Reset output is available for microprocessor systems to insure proper startups. Internal overvoltage and undervoltage comparators on both outputs will pull the $\overline{\text{POR}}$ output low if the output voltages are not within $\pm 8.5\%$. The $\overline{\text{POR}}$ output is delayed by 262,144 clock cycles (about 175ms) after achieving regulation, but will be pulled low immediately when either output is out of regulation.

A High Efficiency 2.5V and 1.8V Step-Down DC/DC Regulator with all Ceramic Capacitors

The low cost and low ESR of ceramic capacitors make them a very attractive choice for use in switching regulators. In addition, ceramic capacitors have a benign failure mechanism unlike tantalum capacitors. Unfortunately, the ESR is so low that it can cause loop stability issues. A solid tantalum capacitor's ESR generates a loop zero at 5kHz–50kHz that can be instrumental in giving acceptable loop phase margin. Ceramic capacitors, on the other hand, remain capacitive to beyond 300kHz and usually resonate

with their ESL before the ESR becomes effective. Also, inexpensive ceramic capacitors are prone to temperature and voltage effects, requiring the designer to check loop stability over the operating temperature range. For these reasons, great care is usually needed when using only ceramic input and output capacitors. The LTC3548 was designed with ceramic capacitors in mind and is internally compensated to handle these difficult design considerations. High quality X5R or X7R ceramic capacitors should be used to minimize the temperature and voltage coefficients.

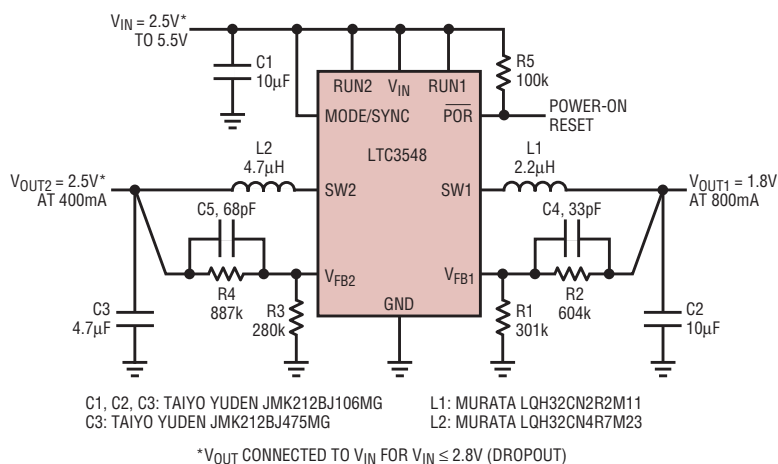



Figure 5. Dual output step-down application yields 1.8V at 800mA and 2.5V at 400mA.

Figure 5 shows a typical application for the LTC3548 using only ceramic capacitors. This circuit provides a regulated 2.5V output and a regulated 1.8V output, at up to 400mA and 800mA, from a 2.5V to 5.5V input.

Conclusion

The LTC3548 is a dual monolithic, step-down regulator that switches at 2.25MHz, minimizing component costs and board real estate requirements for DC/DC regulators. The small size, efficiency, low external component count, and design flexibility of the LTC3548 make it ideal for portable applications. 

Digi-Tune Filters, continued from page 43

can be tuned to 110kHz (maximum $f_0 = 800\text{kHz}/[0.707 \cdot 10]$).


A Tunable Bandpass Filter

The -3dB bandwidth of a second order filter is equal to the center frequency (f_{CENTER}) divided by the Q value (bandwidth = f_{CENTER}/Q). The sensitivity of the second order bandpass filter to the tolerance of the integrator's RC values is proportional to the filter's Q . Typically with a $Q \leq 4$, using a $\pm 1\%$ R and a $\pm 5\%$ C for the filter's two integrators is practical for a second bandpass filter. The sensitivity of the second order bandpass filter with $Q > 4$ increases rapidly for each unit of Q increase and the filter's two integrators should use $\pm 1\%$ RC components.

Figure 4 shows the bandpass filter of Figure 1 tuned from 2kHz to 16kHz using a 2kHz integrator frequency ($R = 205\text{k}, \pm 1\%$ and $C = 390\text{pF}, \pm 5\%$) and an LTC6912-2 with gain settings 1, 2, 4, and 8. The tuned center frequencies responses of Figure 4 are 2.73% lower than the design values of 2kHz, 4kHz, 8kHz and 16kHz and equal to the error of the circuit's RC values of the two integrators (measured values of approximately 206k for each R and 403pF for each C). The gain error at 16kHz is due to the filter's f_0 frequency approaching the maximum f_0 for a $Q = 4$ and a PGA gain equal to 8 (maximum $f_0 = 25\text{kHz} = 800\text{kHz}/[4 \cdot 8]$). The maximum f_0 frequency is a function

of the gain-bandwidth product of the LTC6912-X op amps.

Other Filter Options

Figure 5 shows an example of a second order notch filter. The notch filter's integrator frequency is 500Hz ($1/[2\pi \cdot 316\text{k}\Omega \cdot 1000\text{pF}]$) and with PGA gains 1, 2, 4 and 8 the notch frequency is tuned to 500Hz, 1kHz, 2kHz and 4kHz respectively. Any of the filters discussed above can be made into SPI-tunable fourth order filters by cascading two second order circuits. 

Notes

¹ SPI is a synchronous communication protocol using a 3-wire interface between a microprocessor and a peripheral device