

CMOS Op Amp Outperforms Bipolar Amps in Precision Applications

Introduction

The LTC6081 and LTC6082 are dual and quad low offset, low drift, low noise CMOS operational amplifiers with rail-to-rail input and output stages. Their $0.8\mu\text{V}/^\circ\text{C}$ maximum offset drift, 1pA input bias current, $1.3\mu\text{V}_{\text{pp}}$ of 0.1Hz to 10Hz noise, 120dB open loop gain and 110dB CMRR and PSRR make them perfect for precision applications. The LTC6081 and LTC6082 have a gain bandwidth product of 3.6MHz , with each amplifier only consuming about $330\mu\text{A}$ current for a supply voltage of 2.7 to 5.5V . The 10-lead DFN package of the LTC6081 offers a shutdown function to reduce each amplifier's supply current to $2\mu\text{A}$.

Superior Precision CMOS Op Amp

Bipolar amplifiers can have low offset and low offset drift, but their nA level input bias current make them inappropriate for high input impedance applications such as photodiode amplifiers. CMOS amplifiers usually offer inferior offset drift, CMRR, and PSRR specifications and therefore are not suitable for precision applications. Chopper stabilized amplifiers, also known as zero drift amplifiers, can achieve superior offset and offset drift by means of offset cancellation, but have clock noise and fold-back noise due to sampling. LTC6081 and LTC6082, however, are continuous time CMOS operational amplifiers, which use a patented methodology to improve their offset voltage, offset voltage drift and CMRR. They combine the features of low input bias current, low offset drift and low noise.

Instrumentation Amplifier

Figure 2 shows a typical three op amp instrumentation amplifier. If $R1 = R2$, $R3 = R5$ and $R4 = R6$, then

$$V_{\text{OUT}} = \left(1 + \frac{2R1}{R0}\right) \left(\frac{R5}{R3}\right) (V_{\text{IN2}} - V_{\text{IN1}})$$

by Hengsheng Liu

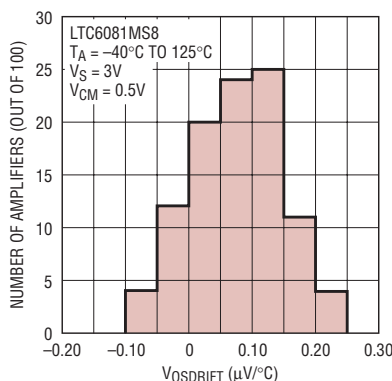


Figure 1. V_{OS} drift histogram of LTC6081

In this two stage structure, the differential voltage passes through the first gain stage with gain of $1 + 2R1/R0$ while the common mode voltage has only unity gain at the first stage, thus improving CMRR. Ratio matching of

$R4/R3$ and $R6/R5$ is critical for CMRR. Gain can be changed by simply changing $R0$ without affecting the resistor matching.

The input referred offset of the amplifier is

$$V_{\text{OS}} = V_{\text{OSB}} - V_{\text{OSA}} + \frac{V_{\text{OSC}}}{1 + \frac{2R1}{R0}}$$

$$\approx V_{\text{OSB}} - V_{\text{OSA}}$$

Statistically, the total V_{OS} is $\sqrt{2}$ times the V_{OS} of a single op amp. Since a single LTC6081 op amp drifts less than $0.8\mu\text{V}/^\circ\text{C}$, the amplifier in Figure 2 will drift less than $1.1\mu\text{V}/^\circ\text{C}$. One drawback of the circuit in Figure 2 is its common mode operating range is no longer rail-to-rail. Assuming

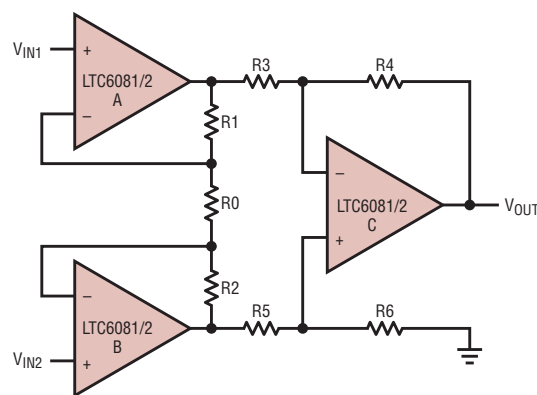


Figure 2. Typical three op amp structure of instrumentation amplifier

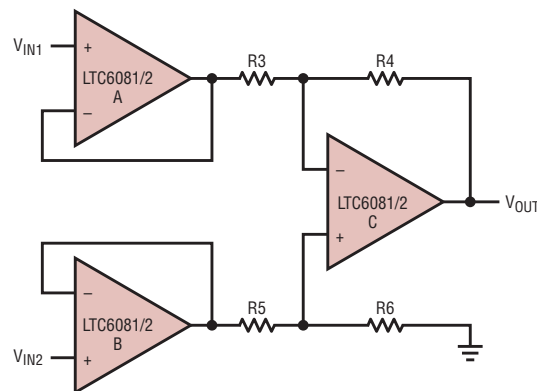


Figure 3. Instrumentation amplifier with unity gain buffers

the differential and common mode input voltage are $V_{IN(DM)}$ and $V_{IN(CM)}$ respectively, the output voltages of op amp A and B are then $V_{IN(CM)} - (2R_1/R_0)V_{IN(DM)}$ and $V_{IN(CM)} + (2R_1/R_0)V_{IN(DM)}$ respectively. So

$$V^- < V_{IN(CM)} \pm \frac{2R_1}{R_0} V_{IN(DM)} < V^+$$

$$V^- + \frac{2R_1}{R_0} V_{IN(DM)} < V_{IN(CM)} <$$

$$V^+ - \frac{2R_1}{R_0} V_{IN(DM)}$$

where V^+ and V^- are the positive and negative supply voltage respectively. The larger the first stage gain or input differential signal is, the narrower the input common mode range is. To widen the input common mode range, the first stage gain can be reduced, but this will compromise CMRR performance.

Figure 3 is a reduced circuit of Figure 2 with a unity gain buffer at the front stage. This circuit can achieve rail-to-rail input range. As mentioned

previously, it won't have the high CMRR of the circuit in Figure 2 since we reduced the front stage gain to unity. If the input resistance requirement can be eased, Figure 3 can be reduced to Figure 4, a single stage difference amplifier. The impedance of the non-inverting and inverting inputs are R_3 and $R_5 + R_6$, respectively. An obvious advantage of the LTC6081 is its super low input bias current. Even with a $1M\Omega$ input resistor R_3 or R_5 , the less than $1pA$ input bias current of LTC6081 will add less than $1\mu V$ to V_{OS} .

The above discussion assumes a perfect matching of R_4/R_3 and R_6/R_5 . If

$$\frac{R_6}{R_5} = (1 + \epsilon) \frac{R_4}{R_3}$$

then the CMRR degrades to

$$20 \log \frac{A_V}{\epsilon}$$

where A_V is the differential gain of the instrumentation amplifier. For example, at gain of 10, to achieve 80dB

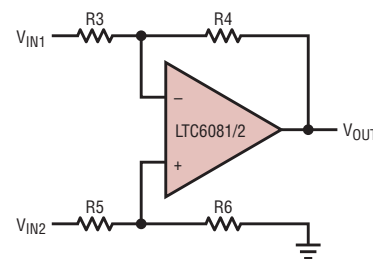



Figure 4. Difference amplifier with no input buffers

CMRR, mismatch of R_4/R_3 and R_6/R_5 should be less than 0.1%. This is true for all the above three circuits. The advantage of the circuit in Figure 2 is that gain can be put at the front stage to ease the matching requirements of the second stage. Matching of R_1 and R_2 in Figure 2 is not important.

Thermocouple Amplifier

Figure 5 shows the LTC6081 in a thermocouple amplifier. The $1M\Omega$ resistors protect the circuit up to $\pm 350V$ with no phase reversal to amplifier output. The $1pA$ maximum I_{BIAS} of the LTC6081 translates to a miniscule $0.05^\circ C$ temperature error with the $1M\Omega$ input protection resistor. The $\pm 90\mu V$ offset over the entire operating temperature range ensures a less than $2^\circ C$ temperature offset.

Conclusion

The LTC6081 and LTC6082 are high performance dual and quad op amps combining excellent noise, offset drift, CMRR, PSRR and input bias current specifications. They perform in a variety of topologies without compromising performance. LTC6081 is available in 8-lead MSOP and 10-lead DFN packages. LTC6082 is available in 16-lead SSOP and DFN packages. 

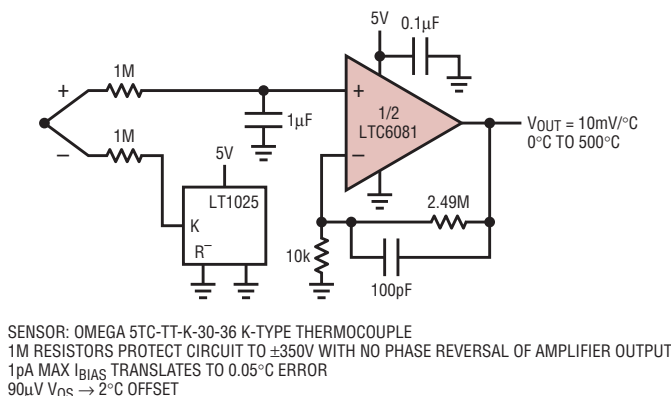


Figure 5. Thermocouple amplifier

LTM4605/07, continued from page 19

Conclusion

The LTM4605 and LTM4607 μ Module regulators simplify the design of buck-boost power supplies. Their low profile $15mm \times 15mm \times 2.8mm$ packages and minimal component count help free up valuable PCB area. High input and high output ratings suit these

regulators to networking, industrial, automotive systems and high power battery-operated devices. Their optimized internal 4-switch architecture provides high efficiency and high performance. Overall, the LTM4605 and LTM4607 reduce product design and test time with a mix of high per-

formance features, flexible settings and ease-of-use. 

Notes

1 For more about layout with Kelvin sense resistors, see "Using Current Sensing Resistors with Hot Swap Controllers and Current Mode Voltage Regulators" by Eric Trelewicz in *Linear Technology Magazine*, September 2003, page 34