

IN THIS ISSUE...

COVER ARTICLE

Two New Controllers for Boost, Flyback, SEPIC and Inverting DC/DC Converters Accept Inputs up to 100V
.....1
Wei Gu

Linear in the News...2

DESIGN FEATURES

Charge Li-Ion Batteries Directly from High Voltage Automotive and Industrial Supplies Using Standalone Charger in a 3mm x 3mm DFN5
Jay Celani

Power Management IC Combines USB On-The-Go and USB Charging in Compact Easy-to-Use Solution8
George H. Barbehenn and Sauparna Das

Power Management IC with Pushbutton Control Generates Six Voltage Rails from USB or 2 AA Cells Via Low Loss PowerPath™ Topology12
John Canfield

Improve Hot Swap Performance and Save Design Time with Hot Swap™ Controller that Integrates 2A MOSFET and Sense Resistor16
David Soo

Compact No R_{SENSE}™ Controllers Feature Fast Transient Response and Regulate to Low V_{OUT} from Wide Ranging V_{IN}18
Terry J. Groom

Space-Saving, Dual Output DC/DC Converter Yields Plus/Minus Voltage Outputs with (Optional) I²C Programming22
Mathew Wich

DESIGN IDEAS

.....26-36
(complete list on page 26)

New Device Cameos37

Design Tools39

Sales Offices40

Two New Controllers for Boost, Flyback, SEPIC and Inverting DC/DC Converters Accept Inputs up to 100V

by Wei Gu

Introduction

Two new versatile DC/DC controller ICs, the LT®3757 and LT3758, are optimized for boost, flyback, SEPIC and inverting converter applications. The LT3757 operates over an input range of 2.9V to 40V, suitable for applications from single-cell lithium-ion battery portable electronics up to high voltage automotive and industrial power supplies. The LT3758 extends the input voltage to 100V, providing flexible, high performance operation in high voltage, high power telecommunications equipment. Both ICs exhibit low shutdown quiescent cur-

rent of 1µA, making them an ideal fit for battery-operated systems.

Both integrate a high voltage, low dropout linear (LDO) regulator. Thanks to a novel FBX pin architecture, the LT3757 and LT3758 can be connected directly to a divider from either the positive output or the negative output to ground. They also pack many popular features such as soft-start, input undervoltage lockout, adjustable frequency and synchronization in a small 10-lead MSOP package or a 3mm x 3mm QFN package.

continued on page 3

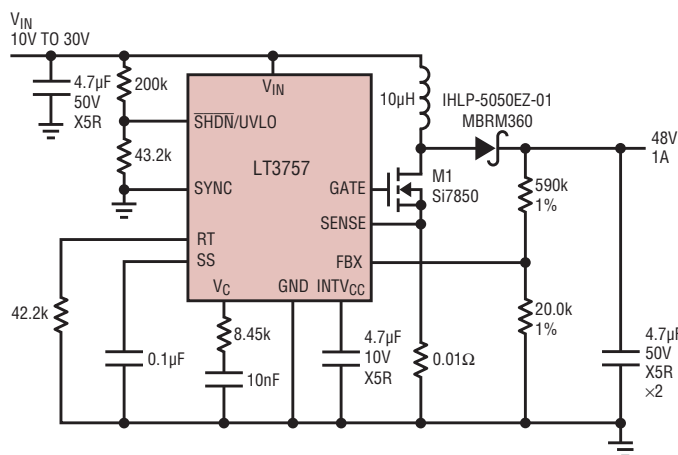


Figure 1. A 10V-30V input, 48V at 1A output boost converter

LT, Linear Express, Linear Technology, LT, LTC, LTM, BodeCAD, Burst Mode, FilterCAD, LTspice, OPTI-LOOP, Over-The-Top, PolyPhase, SwitcherCAD, µModule and the Linear logo are registered trademarks of Linear Technology Corporation. Adaptive Power, Bat-Track, C-Load, DirectSense, Easy Drive, FilterView, Hot Swap, LTBiCMOS, LTCMOS, LinearView, Micropower SwitcherCAD, Multimode Dimming, No Latency ΔE, No Latency Delta-Sigma, No R_{SENSE}, Operational Filter, PanelProtect, PowerPath, PowerSOT, SafeSlot, SmartStart, SNEAK-A-BIT, SoftSpan, Stage Shedding, Super Burst, ThinSOT, TimerBlox, Triple Mode, True Color PWM, UltraFast and VLDO are trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

LT3757/58, continued from page 1

Internal High Voltage LDO

In high voltage applications, the LT3757 and LT3758 eliminate the need for an external regulator or a slow-charge hysteretic start scheme through the integration of an onboard linear regulator, allowing simple start-up and biasing. This regulator generates $INTV_{CC}$, the local supply that runs the IC from the converter input V_{IN} . The internal LDO can operate the IC continuously, provided the input voltage and/or MOSFET gate charge currents are low enough to avoid excessive power dissipation in the part.

When the INTV_{CC} pin is driven externally above its regulated voltage during operation—from the input, the output or a third winding—the internal LDO is automatically turned off, reducing the power dissipation in the IC. The LDO also provides internal current limit function to protect IC from excessive on-chip power dissipation. The current limit decreases as V_{IN} increases. If the current limit is exceeded, the INTV_{CC} voltage falls and triggers the soft-start.

Sensing Output Voltage Made Easier

Unlike traditional controllers, which can only sense positive outputs, the LT3757 and LT3758 have a novel FBX pin architecture that simplifies the design of inverting and non-inverting

converters. The LT3757 and LT3758 each contain two internal error amplifiers; one senses positive outputs and the other negative. When the converter starts switching and the output voltage starts ramping up or down, depending on the topologies, one of the error amplifiers seamlessly takes over the feedback control, while the other becomes inactive.

The FBX pin can be connected directly to a divider from either a positive output or a negative output. This direct connection saves space and expense by eliminating the traditional glue circuitry normally required to level-shift the feedback signal above ground in negative converters. The power supply designer simply decides the output polarity he needs, the topology he wants to use and the LT3757 or LT3758 does the rest.

Precision UVLO Voltage and Soft-Start

Input supply UVLO for sequencing or start-up over-current protection is easily achieved by driving the UVLO with a resistor divider from the V_{IN} supply. The divider output produces 1.25V at the UVLO pin when V_{IN} is at the desired UVLO rising threshold voltage. The UVLO pin has an adjustable input hysteresis, which allows the IC to resist a settable input supply droop before disabling the converter. During a UVLO event, the IC is disabled and V_{IN} quiescent current drops to 1 μ A or lower.

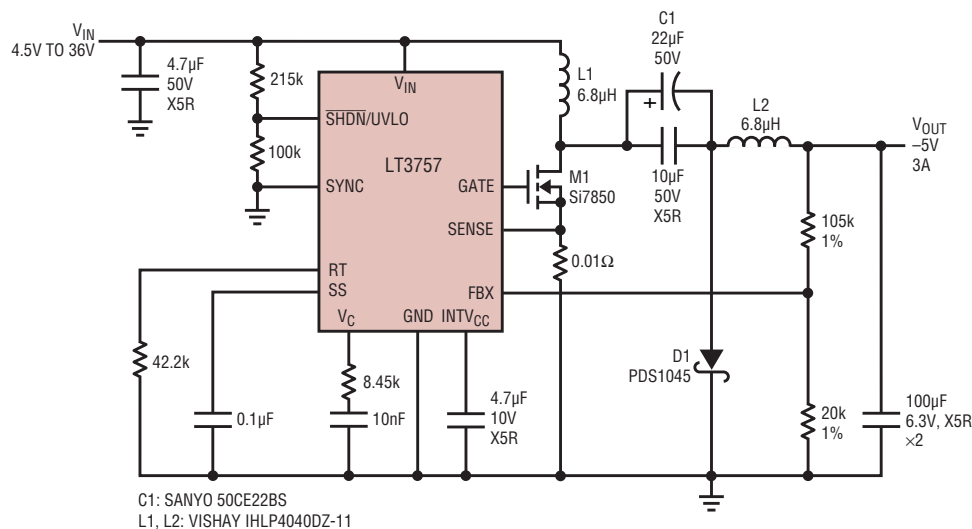


Figure 3. A 4.5V–36V to –5V at 3A inverting converter

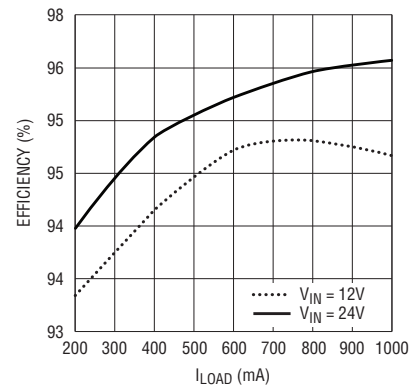


Figure 2. Efficiency of the converter in Figure 1

The SS pin provides access to the soft-start feature, which reduces the peak input current and prevents output voltage overshoot during start-up or recovery from a fault condition. The SS pin reduces the inrush current by not only lowering the current limit but also reducing the switching frequency. In this way soft-start allows the output capacitor to charge gradually towards its final value.

Adjustable/Synchronizable Switching Frequency

The operating frequency of the LT3757 and LT3758 can be programmed from 100kHz to 1MHz range with a single resistor from the R_T pin to ground, or synchronized to an external clock via the SYNC pin.

The adjustable operating frequency allows it to be set outside certain frequency bands to fit applications that are sensitive to spectral noise.

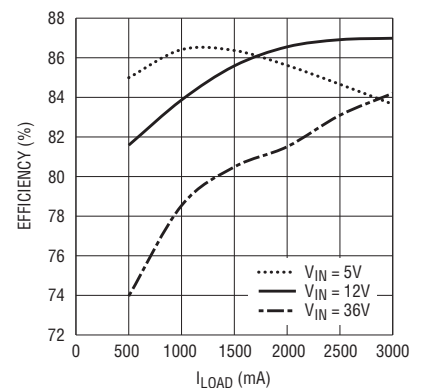


Figure 4. Efficiency of the converter in Figure 3

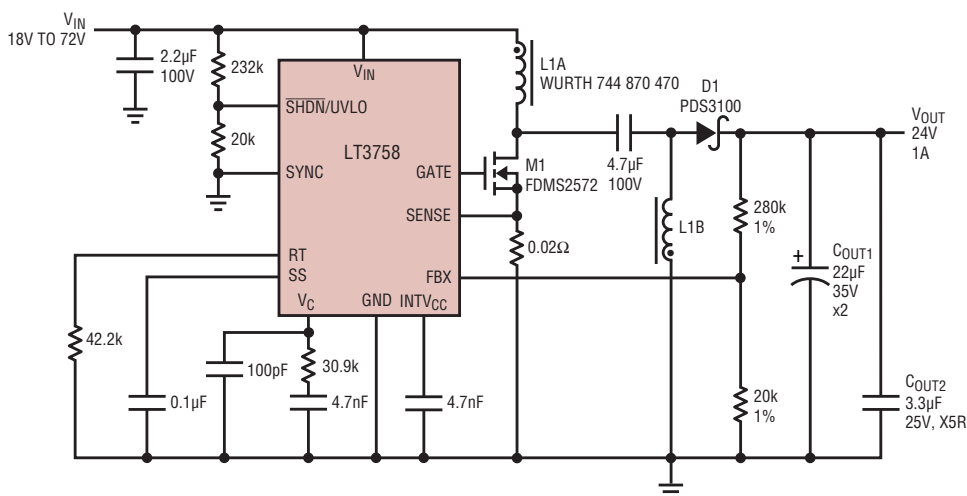


Figure 5. A 18V-72V input, 24V/1A output SEPIC converter

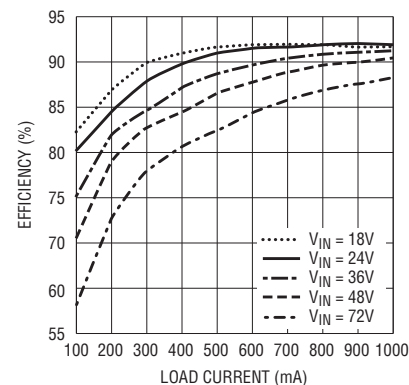


Figure 6. Efficiency of the converter in Figure 5

In space constrained applications, higher switching frequencies can be used to reduce the overall solution size and the output ripple. If power loss is a concern, switching at a lower frequency reduces switching losses, improving efficiency.

Current Mode Control

The LT3757 and LT3758 use a current mode control architecture to enable a higher supply bandwidth, thus improving response to line and load transients. Current mode control also requires fewer compensation components than voltage mode control architectures, making it much easier to compensate over all operating conditions.

A 10V-30V Input, 48V/1A Output Boost Converter

Figure 1 shows a 48V, 1A output converter that takes an input of 10V to 30V. The LT3757 is configured as a boost converter for this applications where the converter output voltage is higher than the input voltage. Figure 2 shows the efficiency for this converter.

A 4.5V-36V Input, -5V/3A Output Inverting Converter

Figure 3 shows the LT3757 in an inverting converter that operates from a 4.5V to 36V input and delivers 3A to a -5V load. The negative output can be either higher or lower in amplitude than the input. It has output short-

circuit protection, which is further enhanced by the frequency foldback feature in the LT3757. The 300kHz operating frequency allows the use of small inductors. The ceramic capacitor used for the DC coupling capacitor provides low ESR and high RMS current capability. The output power can easily scaled by the choice of the components around the chip without modifying the basic design. Figure 4 shows the efficiency for this converter at different input voltages.

An 18V-72V Input, 24V/1A Output SEPIC Converter

A SEPIC converter is similar to the inverting converter in that it can step up or step down the input, but with a positive output. It also offers output

disconnect and short-circuit protection. Figure 5 illustrates an 18V-72V input, 24V/1A output SEPIC power supply using LT3758 as the controller. Figure 6 shows the efficiency for this converter at different input voltages.

An 18V-72V Input, -3.3V/2A Output Flyback Converter

Figure 7 shows the LT3758 in a non-isolated flyback converter with an 18V to 72V input voltage range and a -3.3V / 2A output. It provides robust output short-circuit protection thanks to the frequency foldback feature in the LT3758. The circuit can also be used for different negative voltages simply by changing the value of the resistor divider on the FBX pin.

continued on page 21

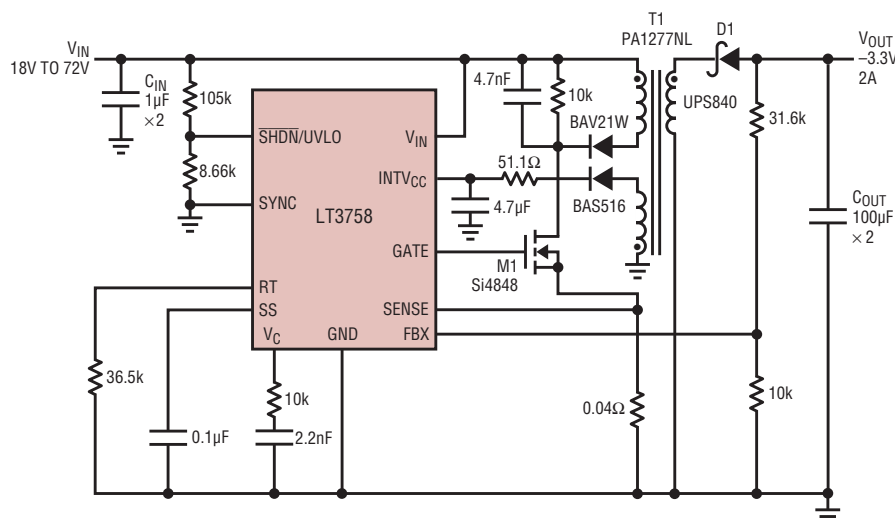


Figure 7. 18V-72V input, -3.3V/2A output flyback converter

